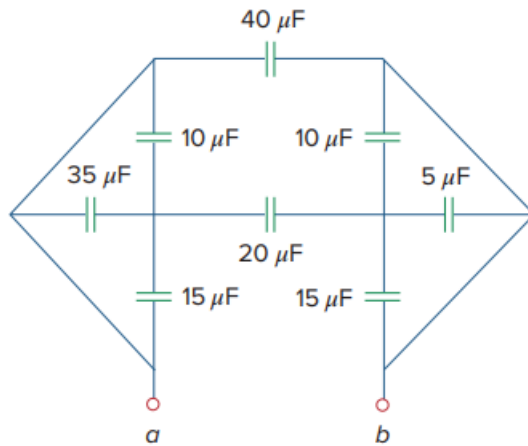


Problem

Obtain the equivalent capacitance of the circuit in Fig. 6.56.


Fig. 6.56:



Step-by-step solution


Step 1 of 6

Given circuit diagram

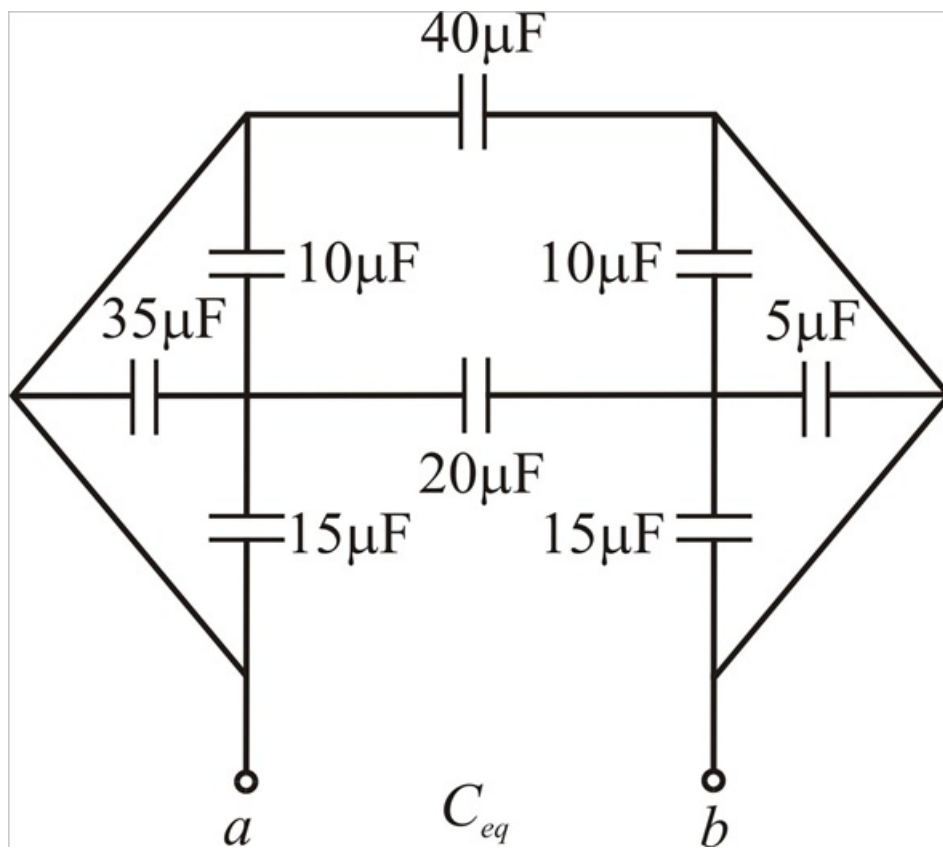

Step 2 of 6

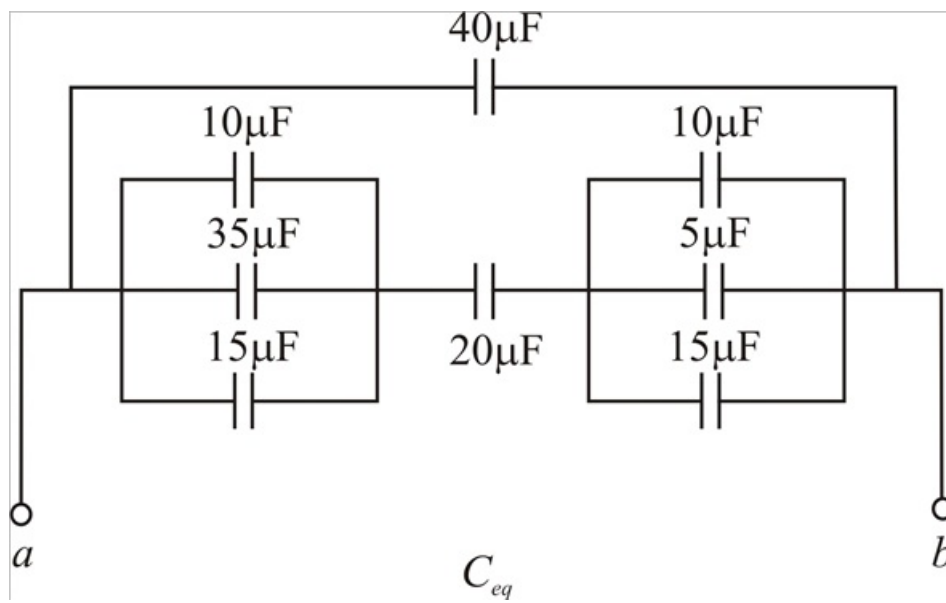Above circuit can be represented as below



Step 3 of 6


In the above circuit $10\mu\text{F}$, $35\mu\text{F}$ and $15\mu\text{F}$ are in parallel

$$10\mu\text{F} + 35\mu\text{F} + 15\mu\text{F} = 60\mu\text{F}$$

In the above circuit $10\mu\text{F}$, $5\mu\text{F}$ and $15\mu\text{F}$ are in parallel

$$10\mu\text{F} + 5\mu\text{F} + 15\mu\text{F} = 30\mu\text{F}$$

Now above circuit reduced to

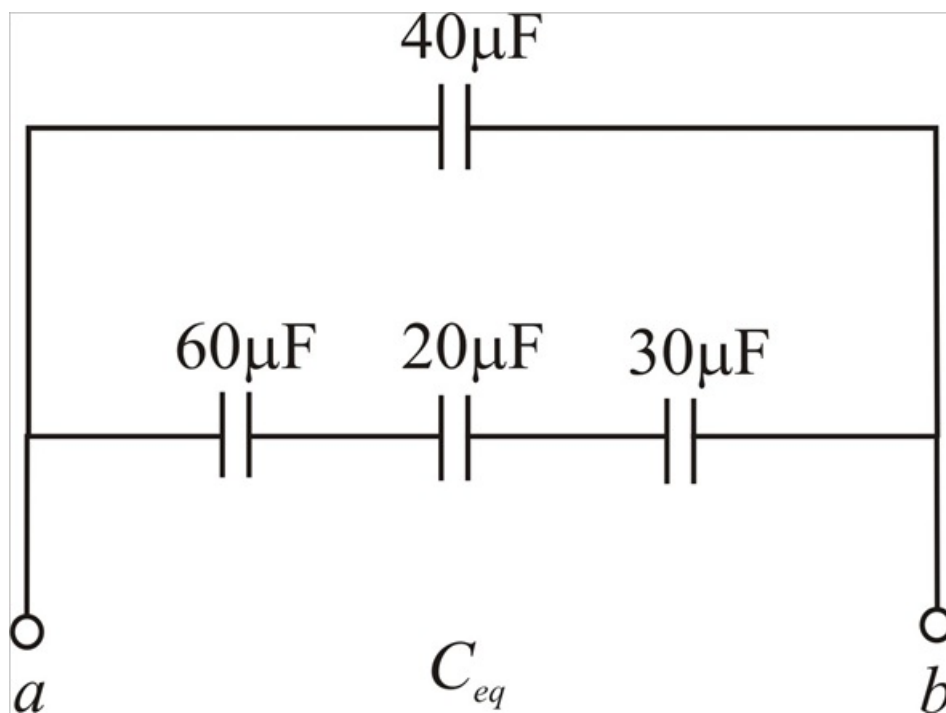

Step 4 of 6

In the above circuit $60\mu\text{F}$, $20\mu\text{F}$ and $30\mu\text{F}$ are in series, so their equivalent capacitance C'_{eq} is

$$C'_{eq} = \frac{1}{\frac{1}{60\mu} + \frac{1}{20\mu} + \frac{1}{30\mu}}$$


$$C'_{eq} = \frac{1}{\frac{1+3+2}{60\mu}}$$

$$C'_{eq} = \frac{60\mu}{6}$$

$$C'_{eq} = 10\mu$$

Step 5 of 6

Above circuit becomes

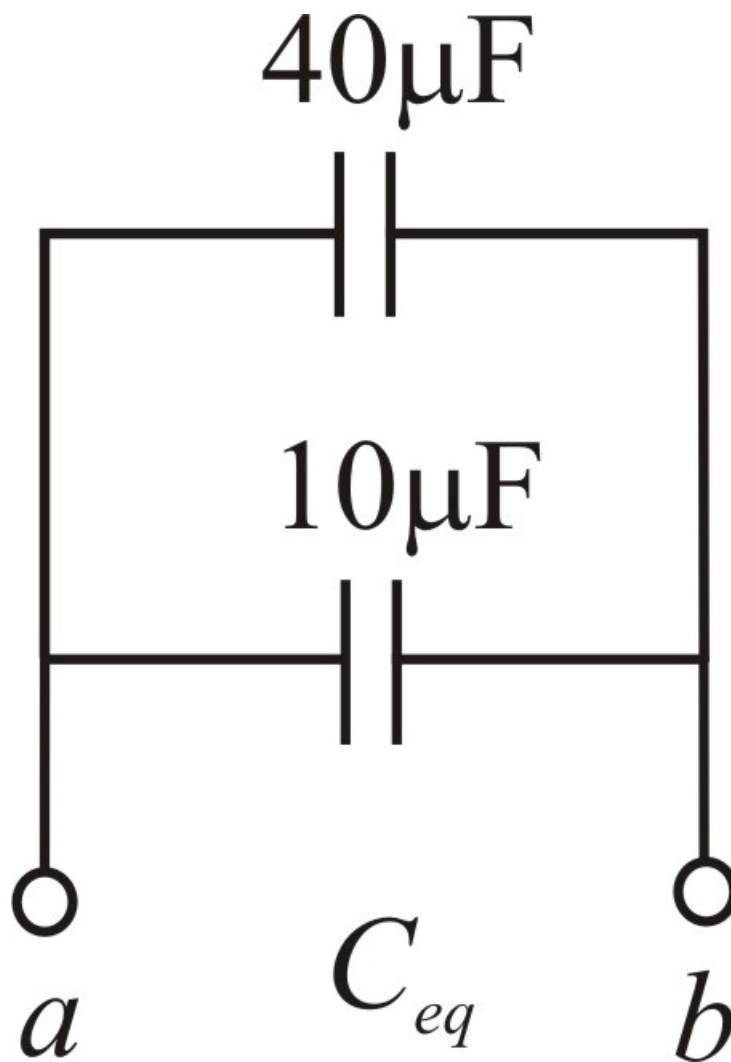

Step 6 of 6

In the above circuit $40\mu\text{F}$ and $10\mu\text{F}$ are in parallel

$$C_{eq} = 40\mu\text{F} + 10\mu\text{F}$$

$$C_{eq} = 50\mu\text{F}$$