

Problem

Given that four $10\text{-}\mu\text{F}$ capacitors can be connected in series and in parallel, find the minimum and maximum values that can be obtained by such series/parallel combinations.

Step-by-step solution

Step 1 of 3

Refer to section 6.3 in the textbook.

Consider the four $10\text{ }\mu\text{F}$ capacitors.

Step 2 of 3

Minimum capacitance can be obtained with the series combination of four capacitors.

Consider the series combination.

Determine the equivalent capacitance of the four $10\text{ }\mu\text{F}$ capacitors connected in series.

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4}$$

Substitute $C_1 = C_2 = C_3 = C_4 = 10\text{ }\mu\text{F}$.

$$\begin{aligned}\frac{1}{C_{eq}} &= \frac{1}{10\text{ }\mu\text{F}} + \frac{1}{10\text{ }\mu\text{F}} + \frac{1}{10\text{ }\mu\text{F}} + \frac{1}{10\text{ }\mu\text{F}} \\ &= \frac{(1+1+1+1)}{10\text{ }\mu\text{F}} \\ &= \frac{4}{10\text{ }\mu\text{F}} \\ &= \frac{2}{5\text{ }\mu\text{F}} \\ C_{eq} &= \frac{5\text{ }\mu\text{F}}{2} \\ &= 2.5\text{ }\mu\text{F}\end{aligned}$$

Thus, the minimum capacitance of the combination is $2.5\text{ }\mu\text{F}$.

Step 3 of 3

Maximum capacitance can be obtained with the parallel combination of four capacitors.

Consider the parallel combination.

Determine the equivalent capacitance of the four $10\text{ }\mu\text{F}$ capacitors connected in parallel.

$$C_{eq} = C_1 + C_2 + C_3 + C_4$$

Substitute $C_1 = C_2 = C_3 = C_4 = 10\text{ }\mu\text{F}$.

$$\begin{aligned}C_{eq} &= 10\text{ }\mu\text{F} + 10\text{ }\mu\text{F} + 10\text{ }\mu\text{F} + 10\text{ }\mu\text{F} \\ &= 40\text{ }\mu\text{F}\end{aligned}$$

Thus, the maximum capacitance of the combination is $40\text{ }\mu\text{F}$.

