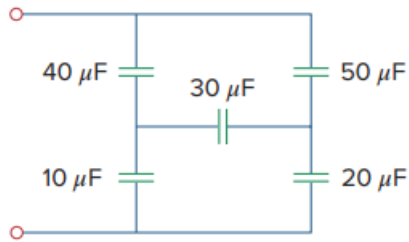


Problem

Obtain the equivalent capacitance of the network shown in c.


Fig. 6.60:



Step-by-step solution

Step 1 of 3

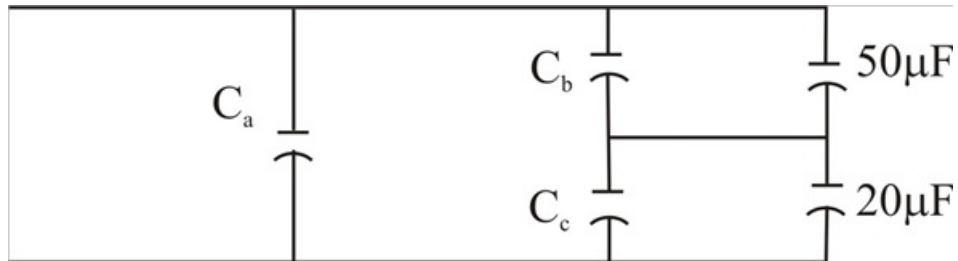We may treat this like A resistive circuit and apply Delta – wye transformation, Except that R is replaced by $1/C$



Step 2 of 3

$$\frac{1}{C_a} = \frac{\left(\frac{1}{10}\right)\left(\frac{1}{40}\right) + \left(\frac{1}{10}\right)\left(\frac{1}{30}\right) + \left(\frac{1}{30}\right)\left(\frac{1}{40}\right)}{\frac{1}{30}}$$

$$= \frac{3}{40} + \frac{1}{10} + \frac{1}{40} = \frac{2}{10}$$

$$C_a = 5 \mu F$$

$$\frac{1}{C_b} = \frac{\frac{1}{400} + \frac{1}{300} + \frac{1}{1200}}{\frac{1}{10}} = \frac{2}{30}$$

$$C_b = 15 \mu F$$

$$\frac{1}{C_c} = \frac{\frac{1}{400} + \frac{1}{300} + \frac{1}{1200}}{\frac{1}{40}} = \frac{4}{15}$$

Step 3 of 3

$$C_c = 3.75 \mu F$$

$$C_b \text{ in parallel with } 50 \mu F = 50 + 15 = 65 \mu F$$

$$C_c \text{ in series with } 20 \mu F = 23.75 \mu F$$

$$65 \text{ in series with } 23.75 \mu F = \frac{65 \times 23.75}{88.75} = 17.39 \mu F$$

$$17.39 \mu F \text{ in parallel with } C_a = 17.39 + 5 = 22.39 \mu F$$

$$\text{Hence } C_{eq} = 22.39 \mu F$$