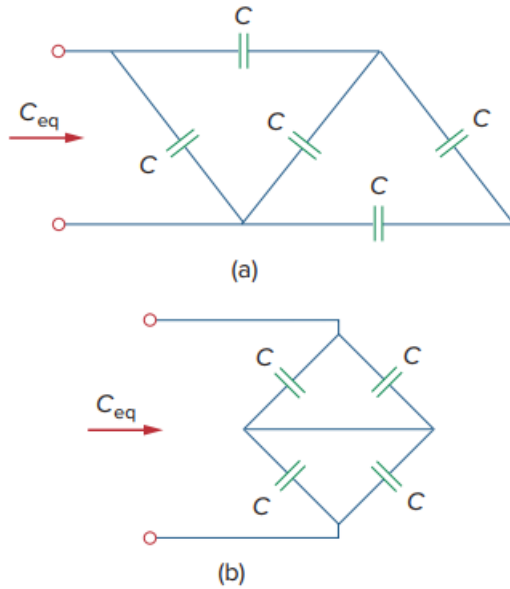


Problem

Determine C_{eq} for each circuit in Fig. 6.61.

Fig. 6.61:



Step-by-step solution

Step 1 of 4

(a)

Refer to Figure 6.61 (a) in the textbook.

In Figure 6.61 (a), the series combination of two capacitors connected in parallel with a capacitor, C . Calculate their equivalent capacitance.

$$\begin{aligned} C_{eq1} &= \left(\frac{C \times C}{C + C} \right) + C \\ &= \frac{C}{2} + C \\ &= \frac{3C}{2} \end{aligned}$$

Draw the reduced circuit of Figure 6.61(a).

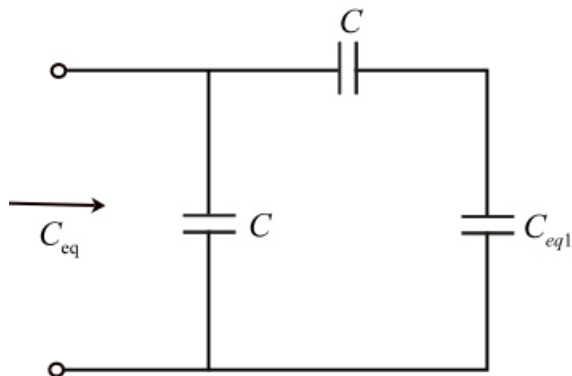


Figure 1

Step 2 of 4

In Figure 1, the capacitors C_{eq1} and C are connected in series and their resultant is in parallel with capacitor, C .

Calculate the equivalent capacitance.

$$\begin{aligned}
 C_{eq} &= \frac{C_{eq1} \times C}{C_{eq1} + C} + C \\
 &= \frac{\frac{3}{2}C \times C}{\frac{3}{2}C + C} + C \\
 &= \frac{\frac{3}{2}C}{\frac{5}{2}} + C \\
 &= \frac{3}{5}C + C \\
 &= \frac{8}{5}C \\
 &= 1.6C
 \end{aligned}$$

Therefore, the equivalent capacitance, C_{eq} is $\boxed{1.6C}$.

Step 3 of 4

(b)

Refer to Figure 6.61 (b) in the textbook.

In Figure 6.61 (b), the capacitors are connected in parallel. Calculate their equivalent capacitances.

$$\begin{aligned}
 C_{eq1} &= C + C \\
 &= 2C \\
 C_{eq2} &= C + C \\
 &= 2C
 \end{aligned}$$

Draw the reduced circuit of Figure 6.61(b).

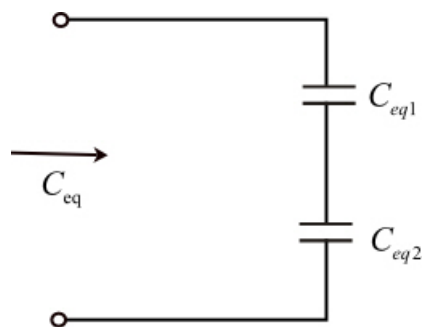


Figure 2

Step 4 of 4

Calculate the equivalent capacitance.

$$\begin{aligned}C_{eq} &= \frac{(C_{eq1}) \times (C_{eq2})}{C_{eq1} + C_{eq2}} \\&= \frac{(2C) \times (2C)}{2C + 2C} \\&= \frac{4C^2}{4C} \\&= C\end{aligned}$$

Therefore, the equivalent capacitance, C_{eq} is .