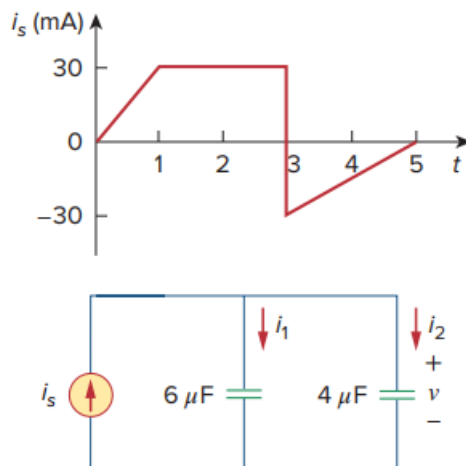


Problem

If $v(0) = 0$, find $v(t)$, $i_1(t)$, and $i_2(t)$ in the circuit of Fig. 6.63.

Fig. 6.63:



Step-by-step solution

Step 1 of 7

Draw the following circuit diagram:

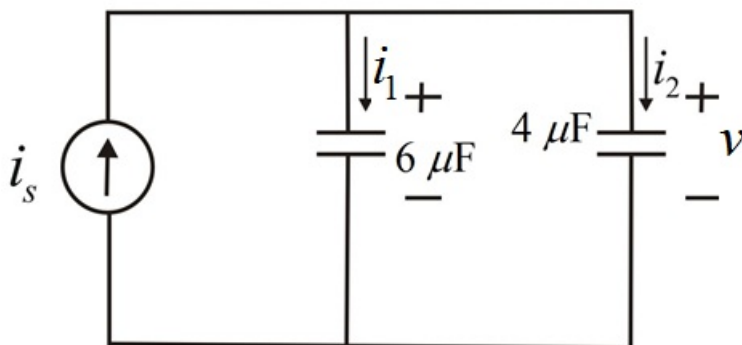


Figure 1

Step 2 of 7

Consider the current waveform is as shown in Figure 2.

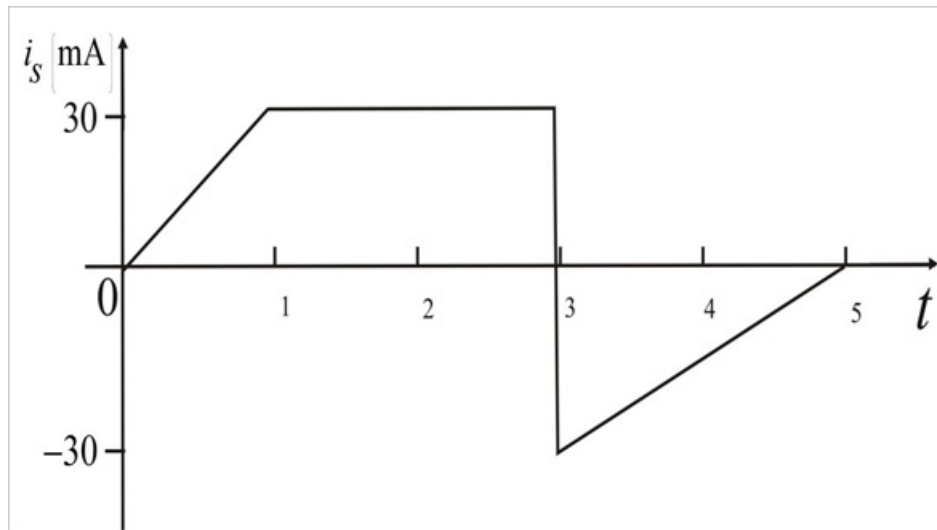


Figure 2

Step 3 of 7

From Figure 2, for $0 < t < 1$, write the line equation.

$$i_s(t) = 30t \text{ A}, 0 < t < 1$$

From Figure 2, for $1 < t < 3$, write the line equation.

$$i_s(t) = 30 \text{ A}, 1 < t < 3$$

From Figure 2, for $3 < t < 5$, write the line equation.

$$\begin{aligned} \frac{y_2 - y_1}{x_2 - x_1} &= \frac{y - y_1}{x - x_1} \\ \frac{0 + 30}{5 - 3} &= \frac{y + 30}{x - 3} \\ 15 &= \frac{y + 30}{x - 3} \\ y &= 15x - 75 \end{aligned}$$

Step 4 of 7

Write the expression for $i_s(t)$.

$$i_s(t) = \begin{cases} 30t \text{ A}, & 0 < t < 1 \\ 30 \text{ A}, & 1 < t < 3 \\ (15t - 75) \text{ A}, & 3 < t < 5 \end{cases}$$

Calculate the value of the current $i_1(t)$.

Apply current division rule across the capacitor $6 \mu\text{F}$ to find $i_1(t)$.

$$i_1(t) = i_s(t) \left(\frac{6 \times 10^{-6}}{4 \times 10^{-6} + 6 \times 10^{-6}} \right) \\ = 0.6i_s(t)$$

Substitute $i_s(t)$ in this expression.

$$i_1(t) = \begin{cases} (30 \times 0.6)t \text{ mA}, & 0 < t < 1 \\ (30 \times 0.6) \text{ mA}, & 1 < t < 3 \\ [(15t - 75) \times 0.6] \text{ mA}, & 3 < t < 5 \end{cases} \\ = \begin{cases} 18t \text{ mA}, & 0 < t < 1 \\ 18 \text{ mA}, & 1 < t < 3 \\ (9t - 45) \text{ mA}, & 3 < t < 5 \end{cases}$$

Therefore, the value of current $i_1(t)$ is $\begin{cases} 18t \text{ mA}, & 0 < t < 1 \\ 18 \text{ mA}, & 1 < t < 3 \\ (9t - 45) \text{ mA}, & 3 < t < 5 \end{cases}$.

Step 5 of 7

Calculate the value of the current $i_2(t)$.

Apply current division rule across the capacitor $4 \mu\text{F}$ to find $i_2(t)$.

$$i_2(t) = i_s(t) \left(\frac{4 \times 10^{-6}}{4 \times 10^{-6} + 6 \times 10^{-6}} \right) \\ i_2(t) = 0.4i_s(t)$$

Substitute $i_s(t)$ in this expression.

$$i_2(t) = \begin{cases} (30 \times 0.4)t \text{ mA}, & 0 < t < 1 \\ (30 \times 0.4) \text{ mA}, & 1 < t < 3 \\ [(15t - 75) \times 0.4] \text{ mA}, & 3 < t < 5 \end{cases} \\ = \begin{cases} 12t \text{ mA}, & 0 < t < 1 \\ 12 \text{ mA}, & 1 < t < 3 \\ (6t - 30) \text{ mA}, & 3 < t < 5 \end{cases}$$

Therefore, the value of current $i_2(t)$ is $\begin{cases} 12t \text{ mA}, & 0 < t < 1 \\ 12 \text{ mA}, & 1 < t < 3 \\ (6t - 30) \text{ mA}, & 3 < t < 5 \end{cases}$.

Step 6 of 7

Calculate the value of the voltage v .

Write the expression for voltage v .

$$v = \frac{1}{C} \int i_2 dt$$

Substitute $i_2(t)$ in this expression.

$$\begin{aligned} v(t) &= \begin{cases} \frac{1 \times 10^{-3}}{4 \times 10^{-6}} \int 12t \text{ V}, 0 < t < 1\text{s} \\ \frac{1 \times 10^3}{4} \int 12 \text{ V}, 1 < t < 3\text{s} \\ \frac{1}{4} \int [6t - 30] \text{ kV}, 3 < t < 5\text{s} \end{cases} \\ &= \begin{cases} 1.5t^2 \text{ kV}, 0 < t < 1\text{s} \\ [3t] \text{ kV} - v(1), 1 < t < 3\text{s} \\ 0.75[t^2] - 7.5[t] - v(3) \text{ kV}, 3 < t < 5\text{s} \end{cases} \\ &= \begin{cases} 1.5t^2 \text{ kV}, 0 < t < 1\text{s} \\ [3t - 15] \text{ kV}, 1 < t < 3\text{s} \\ 0.75t^2 - 7.5t - v(3) \text{ kV}, 3 < t < 5\text{s} \end{cases} \\ &= \begin{cases} \frac{12}{4} \frac{[t^2]}{2} \text{ kV}, 0 < t < 1\text{s} \\ [3t - 1.5] \text{ kV}, 1 < t < 3\text{s} \\ 0.75t^2 - 7.5t - [v(3)] \text{ kV}, 3 < t < 5\text{s} \end{cases} \end{aligned}$$

Step 7 of 7

Simplify voltage v further.

$$\begin{aligned} v(t) &= \begin{cases} \frac{12}{4} \frac{[t^2]}{2} \text{ kV}, 0 < t < 1\text{s} \\ [3t - 1.5] \text{ kV}, 1 < t < 3\text{s} \\ 0.75t^2 - 7.5t - [0.75(3^2) - 7.5(3) - [3(3) - 1.5]] \text{ kV}, 3 < t < 5\text{s} \end{cases} \\ &= \begin{cases} \frac{12}{4} \frac{[t^2]}{2} \text{ kV}, 0 < t < 1\text{s} \\ [3t - 1.5] \text{ kV}, 1 < t < 3\text{s} \\ 0.75t^2 - 7.5t[t] - [-23.25] \text{ kV}, 3 < t < 5\text{s} \end{cases} \\ &= \begin{cases} \frac{12}{4} \frac{[t^2]}{2} \text{ kV}, 0 < t < 1\text{s} \\ [3t - 1.5] \text{ kV}, 1 < t < 3\text{s} \\ 0.75t^2 - 7.5t[t] + 23.25 \text{ kV}, 3 < t < 5\text{s} \end{cases} \end{aligned}$$

Hence, the voltage across the circuit is

$$\begin{cases} \frac{12}{4} \frac{[t^2]}{2} \text{ kV}, 0 < t < 1\text{s} \\ [3t - 1.5] \text{ kV}, 1 < t < 3\text{s} \\ 0.75t^2 - 7.5t[t] + 23.25 \text{ kV}, 3 < t < 5\text{s} \end{cases}$$