

Problem

The current through a 12-mH inductor is $4 \sin 100t$ A. Find the voltage, and the energy stored at $t = \frac{\pi}{200}$ s.

Step-by-step solution

Step 1 of 3

Write the expression of current flowing through inductor.

$$i(t) = 4 \sin(100t) \text{ A}$$

The inductor value is, $L = 12 \text{ mH}$

Determine the voltage across inductor.

$$v = L \frac{di}{dt}$$

Substitute 12 mH for L and $4 \sin(100t)$ A for $i(t)$.

$$\begin{aligned} v &= (12 \times 10^{-3}) \frac{d}{dt} [4 \sin(100t)] \\ &= (12 \times 10^{-3}) [400 \cos(100t)] \\ &= 4.8 \cos(100t) \text{ V} \end{aligned}$$

Voltage at $t = \frac{\pi}{200}$ sec is

$$\begin{aligned} v &= 4.8 \cos\left(100 \times \frac{\pi}{200}\right) \\ v &= 0 \text{ V} \end{aligned}$$

Voltage across inductor at $t = \frac{\pi}{200}$ sec is 0 V

Step 2 of 3

Determine the power in the inductor.

$$p = vi$$

Substitute $4.8 \cos(100t)$ V for v and $4 \sin(100t)$ A for $i(t)$.

$$\begin{aligned} p &= (4.8 \cos(100t)) (4 \sin(100t)) \\ &= 19.2 \cos(100t) \sin(100t) \\ &= \frac{19.2}{2} [2 \cos(100t) \sin(100t)] \\ &= 9.6 [\sin 2(100t)] \quad \quad \quad [\text{Since } 2 \cos(\theta) \sin(\theta) = \sin(2\theta)] \\ p &= 9.6 \sin(200t) \end{aligned}$$

Step 3 of 3

Determine the energy stored in the inductor.

$$\begin{aligned}w &= \int_0^t p dt \\&= \int_0^{\frac{\pi}{200}} 9.6 \sin(200t) dt \\&= \frac{9.6}{200} [-\cos(200t)]_0^{\frac{\pi}{200}} \\&= -\frac{9.6}{200} [\cos(\pi) - \cos(0)] \\&= -\frac{9.6}{200} [-1 - 1] \\&= 0.096 \\&= 96 \text{ mJ}\end{aligned}$$

Therefore, the energy stored in the inductor at $t = \frac{\pi}{200}$ S is 96 mJ.