

Chapter 6, Problem 38P

Problem

The current through a 40-mH inductor is

$$i(t) = \begin{cases} 0, & t < 0 \\ te^{-2t} \text{ A}, & t > 0 \end{cases}$$

Find the voltage $v(t)$.

Step-by-step solution

Step 1 of 1

$$\begin{aligned} V &= L \frac{di}{dt} = 40 \times 10^{-3} (e^{-2t} - 2te^{-2t}) dt \\ &= 40(1 - 2t)e^{-2t} \text{ mV}, t > 0 \end{aligned}$$