

Problem

The voltage across a 50-mH inductor is given by

$$v(t) = [5e^{-2t} + 2t + 4] \text{ V} \quad \text{for } t > 0.$$

Determine the current $i(t)$ through the inductor. Assume that $i(0) = 0 \text{ A}$.

Step-by-step solution

Step 1 of 2

Voltage across inductor is

$$v(t) = [5e^{-2t} + 2t + 4] \text{ V}$$

Current through inductor is

$$i = \frac{1}{L} \int_0^t v(t) dt + i(0)$$

Substitute 50 mH for L and $[5e^{-2t} + 2t + 4] \text{ V}$ for $v(t)$ and 0 A for $i(0)$.

$$= \frac{1}{50 \times 10^{-3}} \int_0^t (5e^{-2t} + 2t + 4) dt + 0$$

Step 2 of 2

Evaluate the integral to get the expression for current .

$$\begin{aligned} &= 20 \left(\frac{5}{-2} e^{-2t} + t^2 + 4t \right) \Bigg|_0^t \\ &= -50e^{-2t} + 20t^2 + 80t - (-50) \\ i &= -50e^{-2t} + 20t^2 + 80t + 50 \text{ A} \end{aligned}$$

Current through 50 mH inductor is $\boxed{-50e^{-2t} + 20t^2 + 80t + 50 \text{ A}}$.