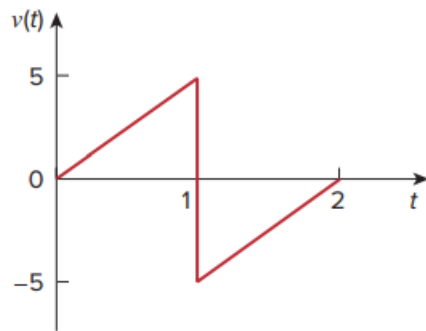


Problem

If the voltage waveform in Fig. 6.68 is applied to a 25-mH inductor, find the inductor current $i(t)$ for $0 < t < 2$ seconds. Assume $i(0) = 0$.

Fig. 6.68:



Step-by-step solution

Step 1 of 3

Refer to voltage waveform in Figure 6.68 in the textbook.

Calculate the voltage equation for $0 < t < 1 \text{ sec}$.

For $0 < t < 1 \text{ sec}$, points are (0,0) (1,5)

Calculate the voltage equation.

$$(v - 0) = \left(\frac{5 - 0}{1 - 0} \right) (t - 0)$$

$$v = 5t \text{ V}$$

Calculate the voltage equation for $1 < t < 2 \text{ sec}$.

For $1 < t < 2 \text{ sec}$, points are (1,-5) (2,0)

$$(v - (-5)) = \left(\frac{0 - (-5)}{2 - 1} \right) (t - 1)$$

$$v + 5 = 5t - 5$$

$$v = 5t - 10 \text{ V}$$

So Inductor voltage is

$$v = \begin{cases} 5t \text{ V} & 0 < t < 1 \\ 5t - 10 \text{ V} & 1 < t < 2 \end{cases}$$

Step 2 of 3

Inductor current at $t = 0$ is zero.

$$i(0) = 0 \text{ A}$$

Calculate the current expression for $0 < t < 1 \text{ sec}$.

$$\begin{aligned} i &= \frac{1}{L} \int_0^t v(t) dt + i(0) \\ &= \frac{1}{25 \times 10^{-3}} \int_0^t 5t dt \\ &= \left(\frac{5}{25 \times 10^{-3}} \right) \frac{t^2}{2} \\ &= 100t^2 \text{ A} \end{aligned}$$

Calculate the current at 1 s.

$$\begin{aligned} i(1 \text{ s}) &= 100(1)^2 \\ &= 100 \text{ A} \end{aligned}$$

Step 3 of 3

Calculate the current expression for $1 < t < 2 \text{ sec}$.

$$\begin{aligned} i &= \frac{1}{L} \int_1^t v(t) dt + i(1) \\ &= \frac{1}{25 \times 10^{-3}} \int_1^t (5t - 10) dt + 100 \\ &= 40 \left(5 \frac{t^2}{2} - 10t \right) \Big|_1^t + 100 \\ &= 40 [2.5t^2 - 10t - (2.5 - 10)] + 100 \\ &= 40 [2.5t^2 - 10t + 7.5] + 100 \\ &= 100t^2 - 400t + 300 + 100 \\ &= 100t^2 - 400t + 400 \text{ A} \end{aligned}$$

Therefore, the inductor current for $0 < t < 2 \text{ sec}$ is,

$$i(t) = \begin{cases} 100t^2 \text{ A} & 0 < t < 1 \text{ sec} \\ 100t^2 - 400t + 400 \text{ A} & 1 < t < 2 \text{ sec} \end{cases}.$$