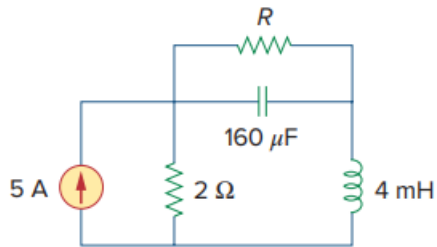


Problem

For the circuit in Fig. 6.70, calculate the value of R that will make the energy stored in the capacitor the same as that stored in the inductor under dc conditions.

Fig. 6.70:



Step-by-step solution

Step 1 of 5

Consider the following circuit:

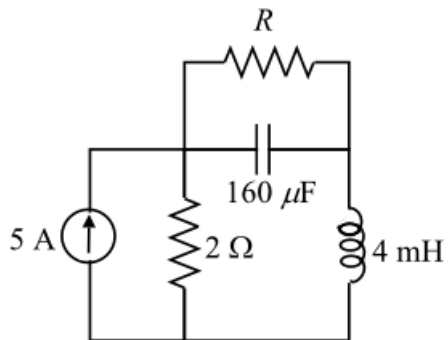


Figure 1

Step 2 of 5

Under dc conditions, the capacitor acts as an open circuit and an inductor acts as a short circuit. Redraw the circuit in Figure 1 under dc conditions.

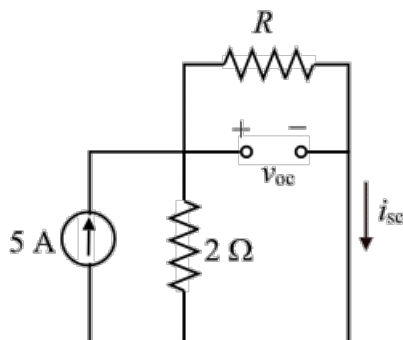


Figure 2

Step 3 of 5

Determine the short circuit current, i_{sc} using current division rule.

$$\begin{aligned} i_{sc} &= (5) \left(\frac{2}{2+R} \right) \\ &= \frac{10}{2+R} \end{aligned}$$

Determine the open circuit voltage, which is the voltage across the resistance R .

$$\begin{aligned} v_{oc} &= i_{sc} R \\ &= \frac{10R}{2+R} \end{aligned}$$

Step 4 of 5

Determine the energy stored in the inductor under dc conditions.

$$\begin{aligned} w_L &= \frac{1}{2} L i_{sc}^2 \\ &= \frac{1}{2} (4 \times 10^{-3}) \left(\frac{10}{2+R} \right)^2 \\ &= \frac{0.2}{(2+R)^2} \end{aligned}$$

Determine the energy stored in the capacitor under dc conditions.

$$\begin{aligned} w_C &= \frac{1}{2} C v_{oc}^2 \\ &= \frac{1}{2} (160 \times 10^{-6}) \left(\frac{10R}{2+R} \right)^2 \\ &= \frac{8 \times 10^{-3} R^2}{(2+R)^2} \end{aligned}$$

Step 5 of 5

To determine the value of R at which the energy stored in the inductor is equal to the energy stored in the capacitor under dc conditions, equate both energies.

$$\begin{aligned} \frac{0.2}{(2+R)^2} &= \frac{8 \times 10^{-3} R^2}{(2+R)^2} \\ 0.2 &= 8 \times 10^{-3} R^2 \\ R^2 &= \frac{0.2}{8 \times 10^{-3}} \\ R^2 &= 25 \\ R &= 5 \, \Omega \end{aligned}$$

Thus, the value of resistance R that makes the energy stored in the capacitor equal to that stored in the inductor under dc conditions is $\boxed{5 \, \Omega}$.