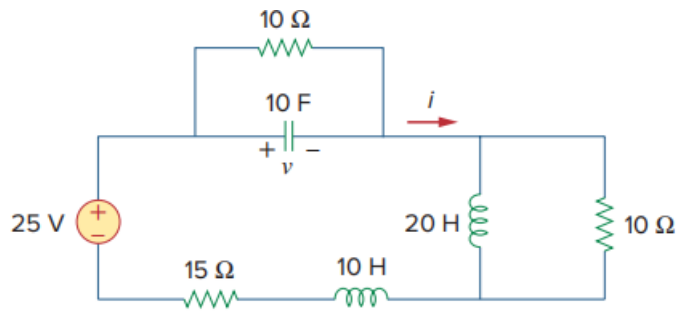


Problem

Under steady-state dc conditions, find i and v in the circuit in Fig. 6.71.

Fig. 6.71:



Step-by-step solution

Step 1 of 3

Under steady state dc condition Inductor acts like short circuit and capacitor acts like open circuit. So the circuit can be modified as


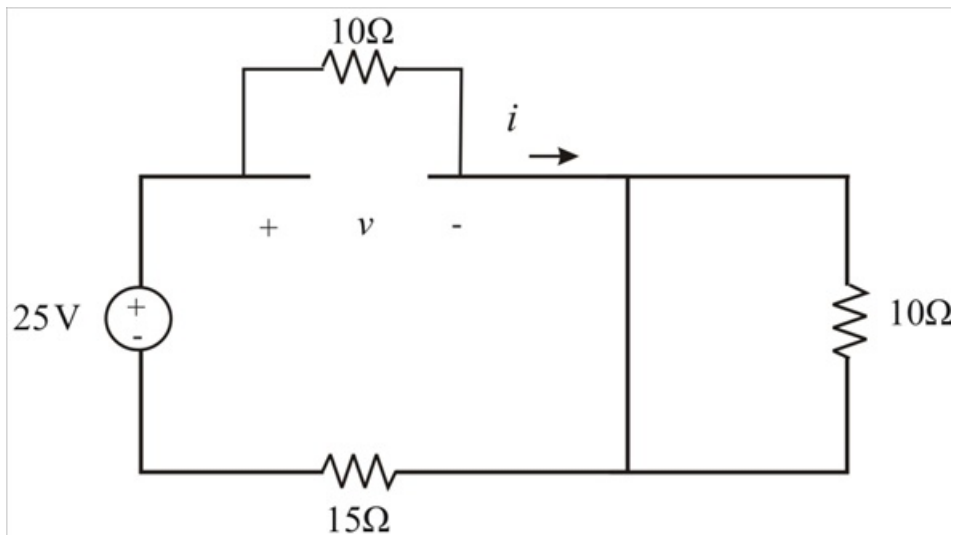


Figure 1

Step 2 of 3

From Figure (1) short circuit is in parallel with 10Ω resistor so remove the 10Ω resistor.

Redraw the circuit:

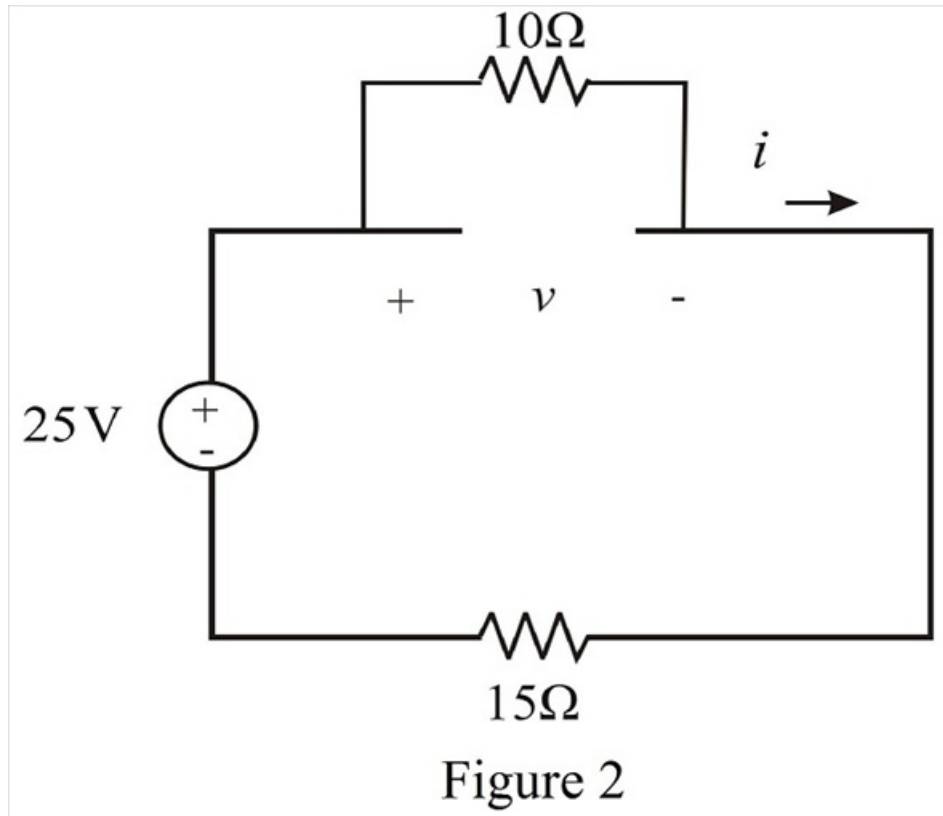

Step 3 of 3

Determine the equivalent resistance of the circuit.

$$\begin{aligned} R_{eq} &= 10\Omega + 15\Omega \\ &= 25\Omega \end{aligned}$$

Calculate the current through the circuit.

$$\begin{aligned} i &= \frac{v}{R_{eq}} \\ i &= \frac{25}{25} \\ i &= 1\text{ A} \end{aligned}$$

Calculate the voltage across the capacitor.

Since, $10\mu\text{F}$ capacitor is parallel with 10Ω resistor. The voltage across the capacitor is same as the voltage across the resistor.

Therefore, the voltage across 10Ω resistor is,

$$\begin{aligned} v &= 10i \\ v &= 10 \times 1 \\ v &= 10\text{ V} \end{aligned}$$

Hence, the voltage and current under steady state dc condition for the given circuit is

$$\begin{aligned} v &= 10\text{ V} \\ i &= 1\text{ A} \end{aligned}$$