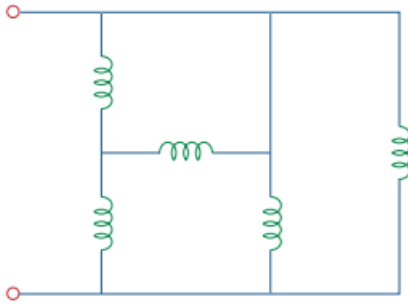


Problem

Find the equivalent inductance of the circuit in Fig. 6.72. Assume all inductors are 40 mH.

Fig. 6.72:




Step-by-step solution

Step 1 of 8

Refer to Figure 6.72 in the text book.

Draw the modified circuit diagram.

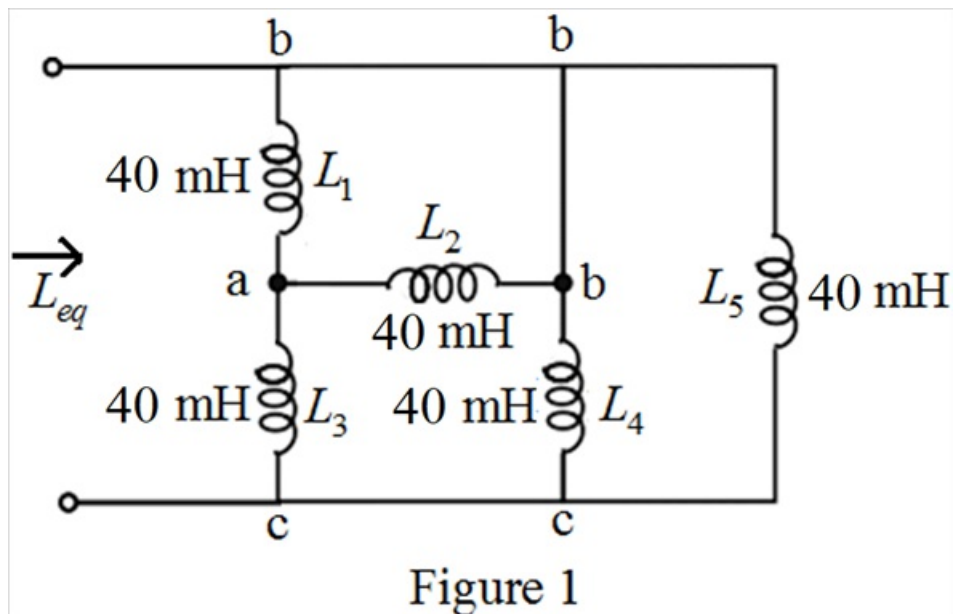

Step 2 of 8

In Figure 1, the inductors L_4 and L_5 are in parallel.

$$\begin{aligned}
 L_{eq1} &= (L_4 \parallel L_5) \\
 &= (40 \times 10^{-3}) \parallel (40 \times 10^{-3}) \\
 &= \frac{(40 \times 10^{-3})(40 \times 10^{-3})}{(40 \times 10^{-3}) + (40 \times 10^{-3})} \\
 &= 20 \times 10^{-3} \\
 L_{eq1} &= 20 \text{ mH}
 \end{aligned}$$

Step 3 of 8

Draw the equivalent circuit diagram.

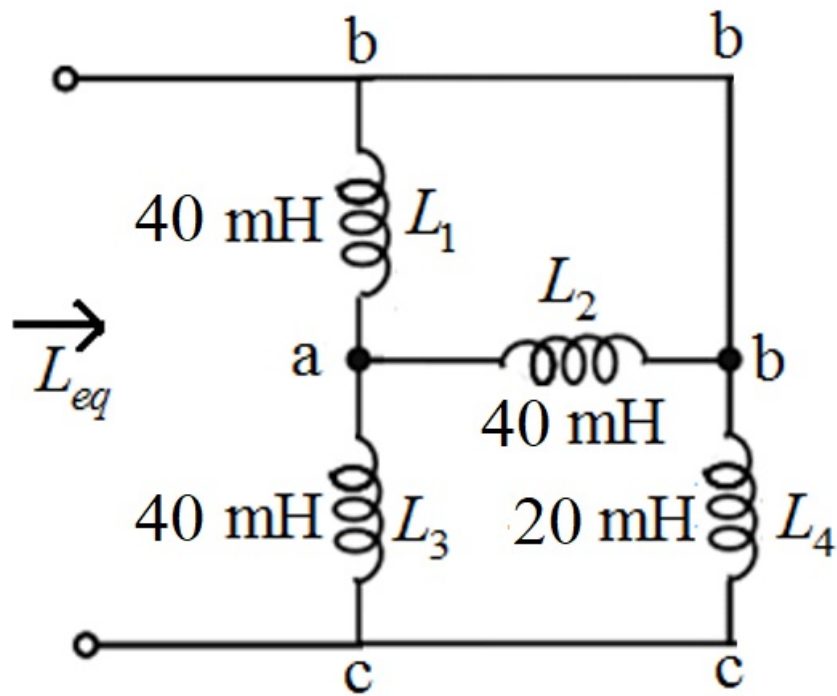


Figure 2

Step 4 of 8

In Figure 2, the inductors L_1 and L_2 are in parallel.

$$\begin{aligned} L_{eq2} &= (L_1 \parallel L_2) \\ &= (40 \times 10^{-3}) \parallel (40 \times 10^{-3}) \\ &= \frac{(40 \times 10^{-3})(40 \times 10^{-3})}{(40 \times 10^{-3}) + (40 \times 10^{-3})} \\ &= 20 \times 10^{-3} \end{aligned}$$

$$L_{eq2} = 20 \text{ mH}$$

Step 5 of 8

Draw the equivalent circuit diagram.

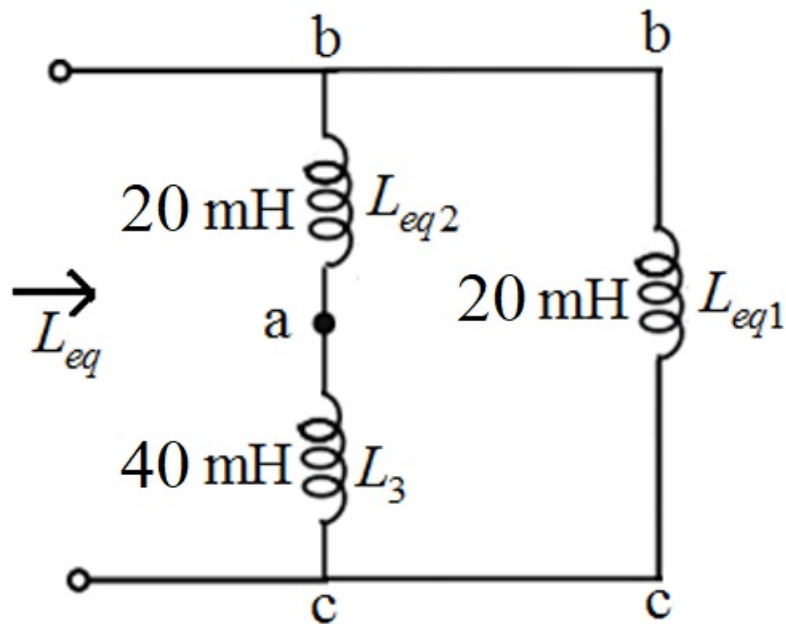


Figure 3

Step 6 of 8

In Figure 3, the inductors L_{eq2} and L_3 are in series.

$$\begin{aligned} L_{eq3} &= L_{eq2} + L_3 \\ &= (20 \times 10^{-3}) + (40 \times 10^{-3}) \\ &= 60 \times 10^{-3} \\ &= 60 \text{ mH} \end{aligned}$$

Step 7 of 8

Draw the equivalent circuit diagram.

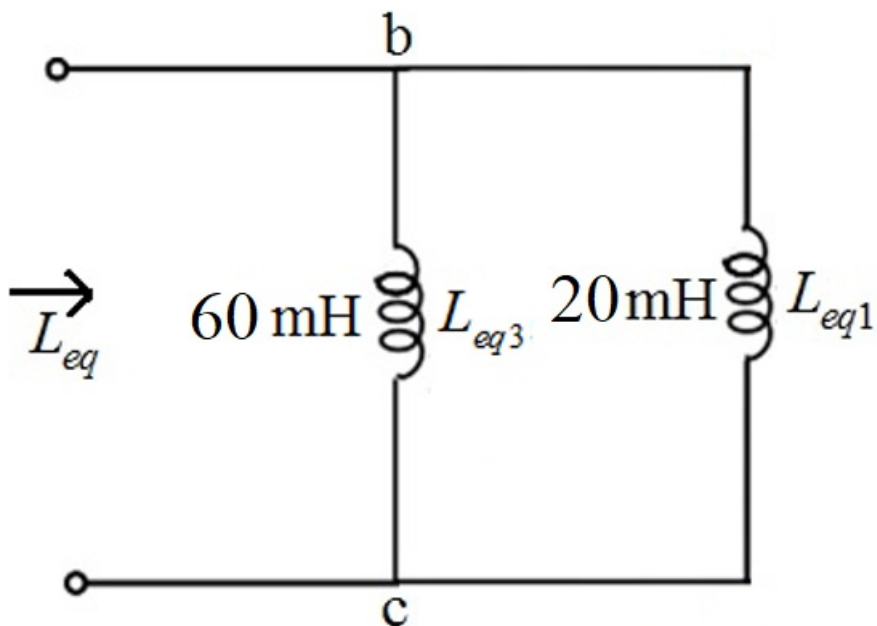


Figure 4

In Figure 4, the inductors L_{eq3} and L_{eq1} are in parallel.

$$\begin{aligned} L_{eq} &= (L_{eq3} \parallel L_{eq1}) \\ &= (60 \times 10^{-3}) \parallel (20 \times 10^{-3}) \\ &= \frac{(60 \times 10^{-3})(20 \times 10^{-3})}{(60 \times 10^{-3}) + (20 \times 10^{-3})} \\ &= 15 \times 10^{-3} \end{aligned}$$

$$L_{eq} = 15 \text{ mH}$$

Thus, the equivalent inductance of the circuit is 15 mH.