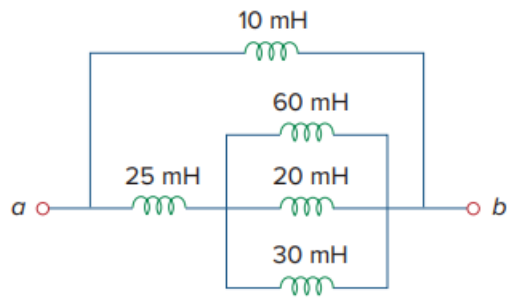


Problem

Determine L_{eq} at terminals a - b of the circuit in Fig. 6.73.

Fig. 6.73:



Step-by-step solution

Step 1 of 1

From the given circuit diagram

$$L_{eq} = 10\text{m} \parallel [25\text{m} + (60\text{m} \parallel 20\text{m} \parallel 30\text{m})]$$

$$L_{eq} = 10\text{m} \parallel [25\text{m} + 10\text{m}]$$

$$L_{eq} = 10\text{m} \parallel 35\text{m}$$

$$L_{eq} = 7.7777\text{m}$$

$$\boxed{L_{eq} = 7.778\text{mH}}$$