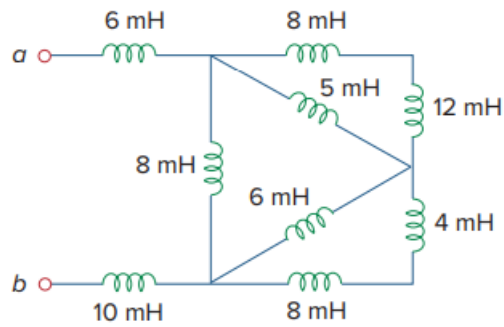


Problem

Find L_{eq} at the terminals of the circuit in Fig. 6.75.

Fig. 6.75:



Step-by-step solution

Step 1 of 5

Refer to the circuit diagram depicted in Figure 6.75 in the textbook.

It is clear that, in Figure 6.75, at extreme right end inductors 8 mH and 12 mH are connected in series. Similarly, inductors 8 mH and 4 mH are connected in series.

The equivalent inductances are,

$$\Rightarrow 8\text{ mH} + 12\text{ mH}$$


$$\Rightarrow 20\text{ mH}$$

And

$$\Rightarrow 8\text{ mH} + 4\text{ mH}$$

$$\Rightarrow 12\text{ mH}$$

Draw the modified circuit diagram.

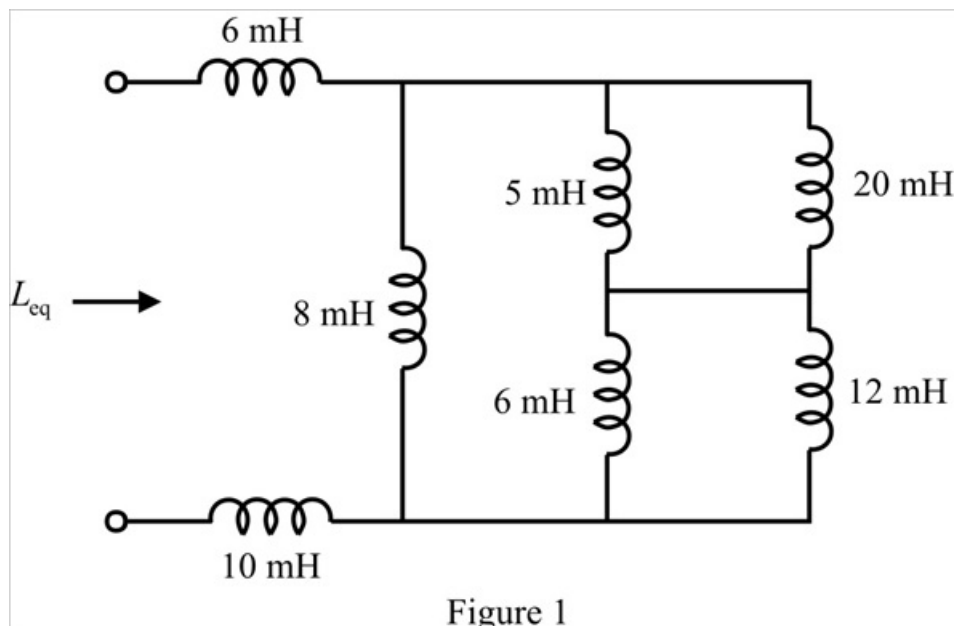

Step 2 of 5

In Figure 1, the inductors 5 mH and 20 mH are connected in parallel. Find its equivalent inductance.

$$\Rightarrow 5 \parallel 20$$

$$\Rightarrow \frac{5 \times 20}{5 + 20}$$

$$\Rightarrow 4 \text{ mH}$$

Similarly, the inductors 6 mH and 12 mH are connected in parallel. Find its equivalent inductance.


$$\Rightarrow 6 \parallel 12$$

$$\Rightarrow \frac{6 \times 12}{6 + 12}$$

$$\Rightarrow 4 \text{ mH}$$

Step 3 of 5

Draw the reduced circuit diagram.

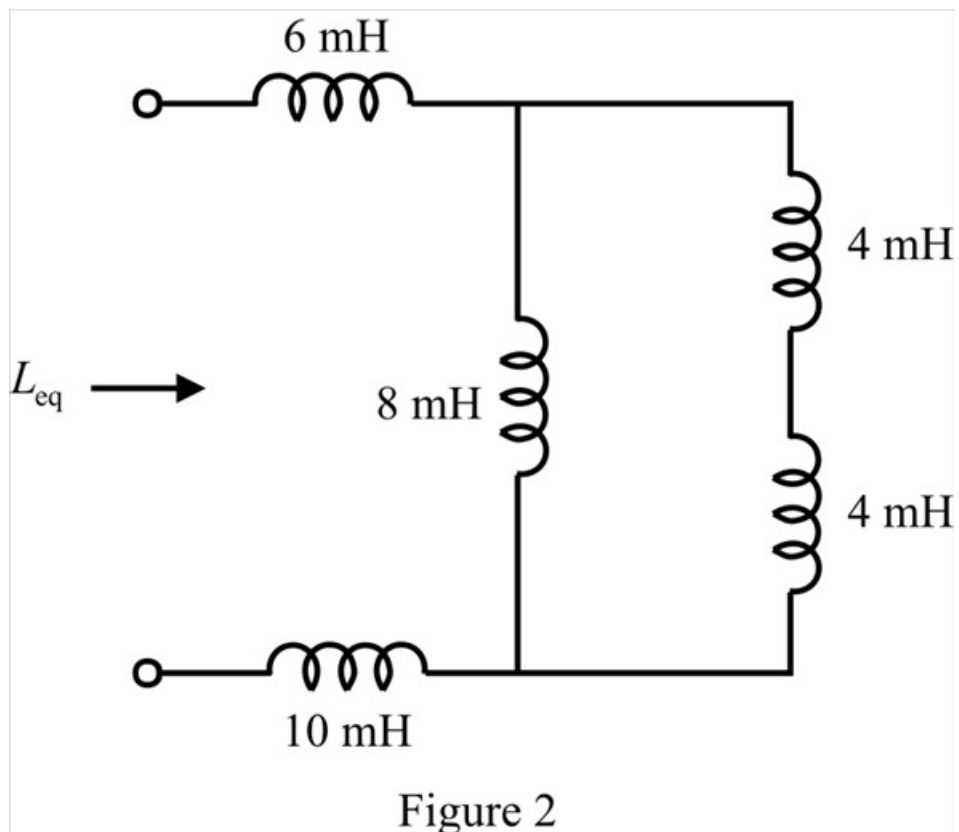

Step 4 of 5

In Figure 2, the series combination of two 4 mH inductors is in parallel with 8 mH inductor. Determine its equivalent inductance.


$$\Rightarrow 8 \parallel (4+4)$$

$$\Rightarrow 8 \parallel 8$$

$$\Rightarrow \frac{8 \times 8}{8+8}$$

$$\Rightarrow 4 \text{ mH}$$

Draw the modified circuit diagram.

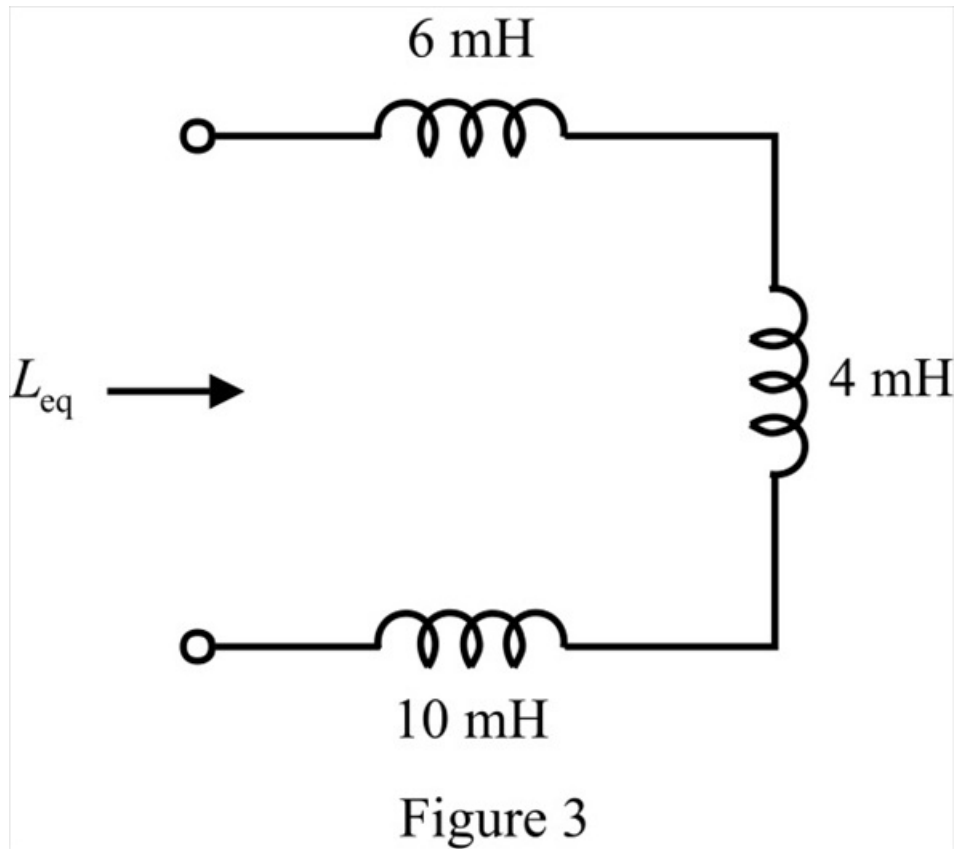

Step 5 of 5

In Figure 3, the three inductors are connected in series. Calculate the equivalent inductance.

$$L_{eq} = 6 + 4 + 10$$

$$= 20 \text{ mH}$$

Therefore, the equivalent inductance of the circuit is 20 mH.