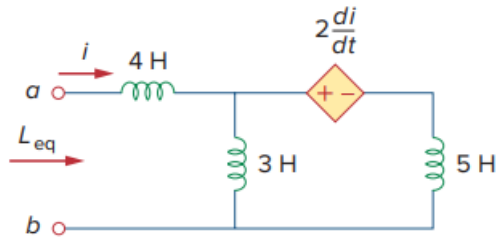


Problem

Determine L_{eq} that may be used to represent the inductive network of Fig. 6.79 at the terminals.

Fig. 6.79:



Step-by-step solution

Step 1 of 4

Refer to Figure 6.79 in the textbook.

Represent the voltages and currents and redraw the circuit.

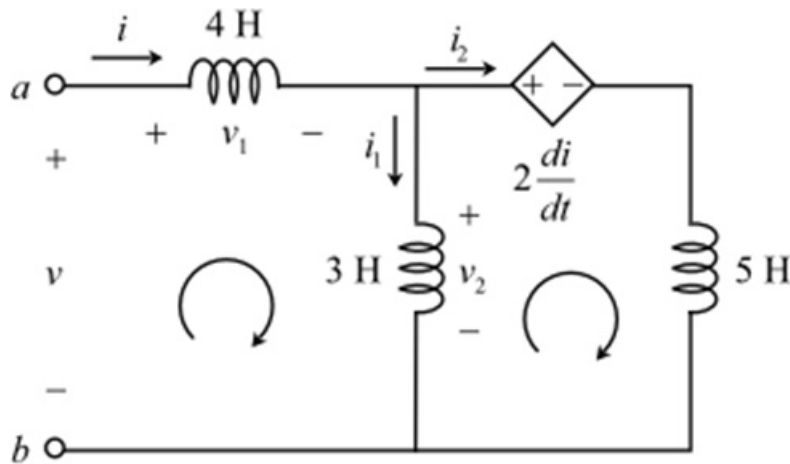


Figure 1

Step 2 of 4

Find the equivalent inductance of the circuit.

Apply Kirchhoff's voltage law to the first loop of the circuit.

$$\begin{aligned} v &= v_1 + v_2 \\ &= (4 \text{ H}) \frac{di}{dt} + v_2 \end{aligned}$$

Write the expression for the voltage v_2 .

$$\begin{aligned} v_2 &= (3 \text{ H}) \frac{di_1}{dt} \\ \frac{di_1}{dt} &= \frac{v_2}{3} \end{aligned}$$

Step 3 of 4

Apply Kirchhoff's voltage law to the second loop of the circuit.

$$-v_2 + 2 \frac{di}{dt} + (5 \text{ H}) \frac{di_2}{dt} = 0$$

$$\begin{aligned} v_2 &= 2 \frac{di}{dt} + 5 \frac{di_2}{dt} \\ &= 2 \frac{di}{dt} + 5 \frac{d}{dt}(i - i_1) \quad (\text{since, } i = i_1 + i_2) \\ &= 2 \frac{di}{dt} + 5 \frac{di}{dt} - 5 \frac{di_1}{dt} \\ &= 7 \frac{di}{dt} - 5 \frac{di_1}{dt} \end{aligned}$$

Substitute the expression of the differentiation of i_1 in the equation.

$$\begin{aligned} v_2 &= 7 \frac{di}{dt} - 5 \left(\frac{v_2}{3} \right) \quad \left(\text{since, } \frac{di_1}{dt} = \frac{v_2}{3} \right) \\ v_2 + \frac{5}{3} v_2 &= 7 \frac{di}{dt} \\ v_2 \left(1 + \frac{5}{3} \right) &= 7 \frac{di}{dt} \\ 2.67 v_2 &= 7 \frac{di}{dt} \end{aligned}$$

Step 4 of 4

Simplify the expression further.

$$\begin{aligned} v_2 &= \left(\frac{7}{2.67} \right) \frac{di}{dt} \\ &= 2.625 \frac{di}{dt} \end{aligned}$$

Substitute this expression of v_2 in the equation of v .

$$\begin{aligned} v &= 4 \frac{di}{dt} + v_2 \\ &= 4 \frac{di}{dt} + 2.625 \frac{di}{dt} \\ &= \frac{di}{dt} (4 + 2.625) \\ &= 6.625 \frac{di}{dt} \end{aligned}$$

The general expression for the input voltage is,

$$v = L_{eq} \frac{di}{dt}$$

Compare this expression with the voltage equation obtained. Therefore,

$$L_{eq} = 6.625 \text{ H}$$

Therefore, the equivalent inductance of the circuit is, 6.625 H.