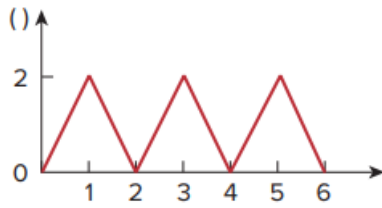


## Problem

The current waveform in Fig. 6.80 flows through a 3-H inductor. Sketch the voltage across the inductor over the interval  $0 < t < 6$  s.

**Fig. 6.80:**



## Step-by-step solution

## Step 1 of 1

$$V = L \frac{di}{dt} = 3 \frac{di}{dt} = 3 \times \text{Slope of } i(t)$$

Thus  $V$  is sketched below:

