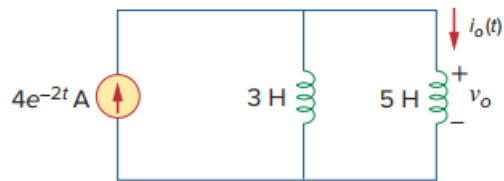


Problem

In the circuit of Fig. 6.82, $i_o(0) = 2$ A. Determine $i_o(t)$ and $v_o(t)$ for $t > 0$.

Fig. 6.82:



Step-by-step solution

Step 1 of 2

Refer to the circuit diagram depicted in Figure 6.82 in the textbook.

The value of source current is, $i_s(t) = 4e^{-2t}$ V

In Figure 6.82, two inductors are connected in parallel. Find its equivalent inductance.

$$\begin{aligned} L_{\text{eq}} &= 3 \parallel 5 \\ &= \frac{3 \times 5}{3 + 5} \\ &= \frac{15}{8} \text{ H} \end{aligned}$$

Determine the voltage, $v_o(t)$.

$$\begin{aligned} v_o(t) &= L_{\text{eq}} \frac{di_s(t)}{dt} \\ &= \frac{15}{8} \frac{d}{dt} (4e^{-2t}) \\ &= \frac{15}{8} (-4 \times 2e^{-2t}) \\ &= -15e^{-2t} \text{ V} \end{aligned}$$

Therefore, the voltage $v_o(t)$ is $\boxed{-15e^{-2t} \text{ V}}$.

Step 2 of 2

Determine the current, $i_o(t)$ through 5 H inductor.

$$i_o(t) = \frac{1}{L} \int_0^t v_o(t) dt + i_o(0)$$

$$= \frac{1}{5} \int_0^t -15e^{-2t} dt + 2$$

$$= \frac{-15}{5} \int_0^t e^{-2t} dt + 2$$

$$= -3 \left(\frac{e^{-2t}}{-2} \right) \Big|_0^t + 2$$

$$= 1.5(e^{-2t} - 1) + 2$$

$$= 1.5e^{-2t} - 1.5 + 2$$

$$= 1.5e^{-2t} + 0.5\text{ A}$$

Therefore, the current $i_o(t)$ is $\boxed{1.5e^{-2t} + 0.5\text{ A}}$.