

Problem


The switch in Fig. 6.86 has been in position A for a long time. At $t = 0$, the switch moves from position A to B. The switch is a make-before-break type so that there is no interruption in the inductor current. Find:

(a) $i(t)$ for $t > 0$,

(b) v just after the switch has been moved to position B,

(c) $v(t)$ long after the switch is in position B.

Fig. 6.86:

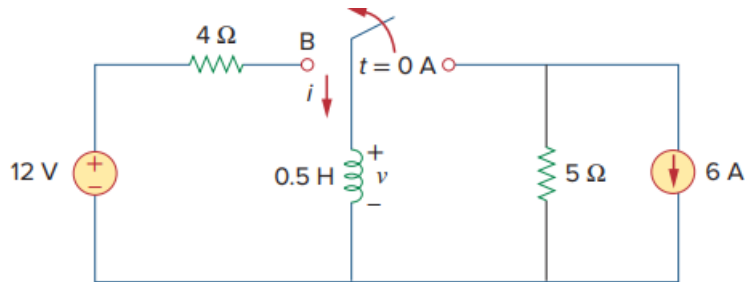

Step-by-step solution

Step 1 of 10

(a)

Refer to the Figure 6.86 in the text book.

At $t < 0$ s, the switch is closed at position A.

Draw the following circuit diagram for $t < 0$ s.

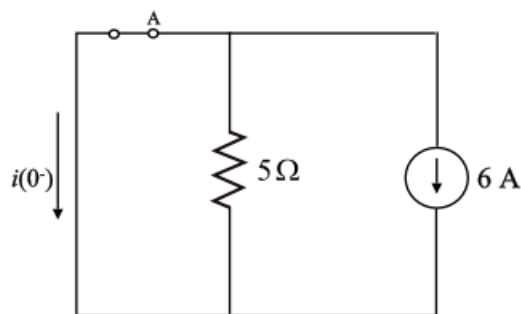


Figure 1

Step 2 of 10

Determine the value of current $i(0^-)$ using Figure 1.

$$i(0^-) = -6 \text{ A} \quad [\text{Since short circuit}]$$

Step 3 of 10

At $t = 0\text{ s}$, the switch is closed at position B.

Draw the following circuit diagram for $t = \infty\text{ s}$.

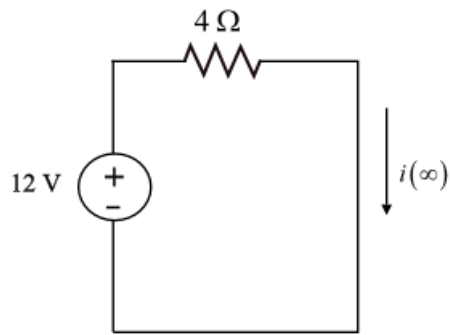


Figure 2

Step 4 of 10

Determine the value of current $i(\infty)$ using Figure 2.

$$\begin{aligned} i(\infty) &= \frac{12\text{ V}}{4\Omega} \\ &= 3\text{ A} \end{aligned}$$

Step 5 of 10

Draw the following circuit diagram for $t = 0\text{ s}$.

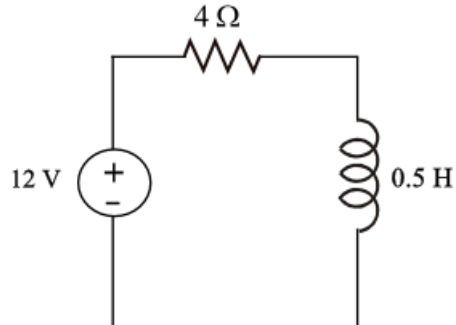


Figure 3

Step 6 of 10

Determine the value of time constant using Figure 3.

$$\begin{aligned} \tau &= \frac{L}{R} \\ &= \frac{0.5}{4} \\ &= \frac{1}{8}\text{ s} \end{aligned}$$

Step 7 of 10

Determine the current flowing thorough the inductor for $t > 0$.

$$\begin{aligned} i(t) &= i(\infty) + [i(0) - i(\infty)]e^{\frac{-t}{\tau}} \\ &= 3 + [-6 - 3]e^{\frac{-t}{\left(\frac{1}{8}\right)}} \\ i(t) &= 3 - 9e^{-8t} \text{ A} \end{aligned}$$

Therefore, the current flowing thorough the inductor for $t > 0$ is $i(t) = 3 - 9e^{-8t} \text{ A}$.

Step 8 of 10

(b)

It is known that, the current inductor does not change instantaneously.

Draw the following circuit diagram for $t = 0 \text{ s}$.

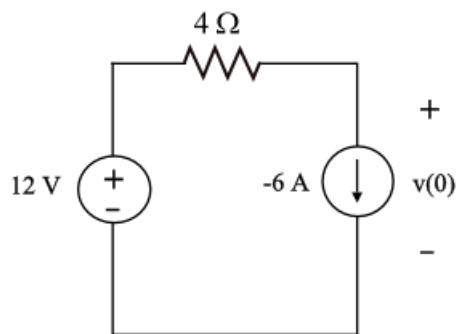


Figure 4

Step 9 of 10

Apply kirchoffs voltage law in Figure 4.

$$\begin{aligned} -12 + (4\Omega)(-6 \text{ A}) + v(0) &= 0 \\ -12 - 24 + v(0) &= 0 \\ v(0) &= 36 \text{ V} \end{aligned}$$

Therefore, the voltage across inductor after switch has moved to position B is 36 V .

Step 10 of 10

(c)

Determine the voltage across inductor after the switch is in position B.

$$\begin{aligned} v(t) &= L \frac{di(t)}{dt} \\ &= (0.5) \frac{d}{dt} [3 - 9e^{-8t} \text{ A}] \\ &= (0.5) [0 + 72e^{-8t} \text{ V}] \\ &= 36e^{-8t} \text{ V} \end{aligned}$$

Therefore, the voltage across inductor after the switch is in position B is $v(t) = 36e^{-8t} \text{ V}$.