

Problem

The current $i(t)$ through a 20-mH inductor is equal, in magnitude, to the voltage across it for all values of time. If $i(0) = 2$ A, find $i(t)$.

Step-by-step solution

Step 1 of 1

Given

$$L = 20\text{mH}; i(0) = 2\text{A}$$

$$i(t) = v(t) \quad \text{-----}(1)$$

$$\text{We know } v(t) = L \frac{di(t)}{dt} \quad \text{-----}(2)$$

(1) into (2):

$$i(t) = L \frac{di(t)}{dt}$$

$$\frac{1}{i(t)} di(t) = \frac{1}{L} dt$$

By taking integration on both sides

$$\int_0^t \frac{1}{i(t)} di(t) = \frac{1}{L} \int_0^t 1 dt$$

$$[\ln i(t)]_0^t = \frac{1}{L} [t]_0^t$$

$$\ln i(t) - \ln i(0) = \frac{t}{L}$$

$$\ln i(t) - \ln i(0) = \ln \left[e^{\frac{t}{L}} \right]$$

$$\ln i(t) - \ln(2) = \ln \left[e^{50t} \right]$$

$$\ln i(t) = \ln \left[2e^{50t} \right]$$

$$i(t) = 2e^{50t} \text{ A}$$