

Chapter 6, Problem 68P

Problem

A 6-V dc voltage is applied to an integrator with $R = 50 \text{ k}\Omega$, $C = 100 \text{ }\mu\text{F}$ at $t = 0$. How long will it take for the op amp to saturate if the saturation voltages are +12 V and -12 V? Assume that the initial capacitor voltage was zero.

Step-by-step solution

Step 1 of 3

Refer to section 6.6 in the textbook.

Consider the following integrator circuit diagram as shown in Figure 1.

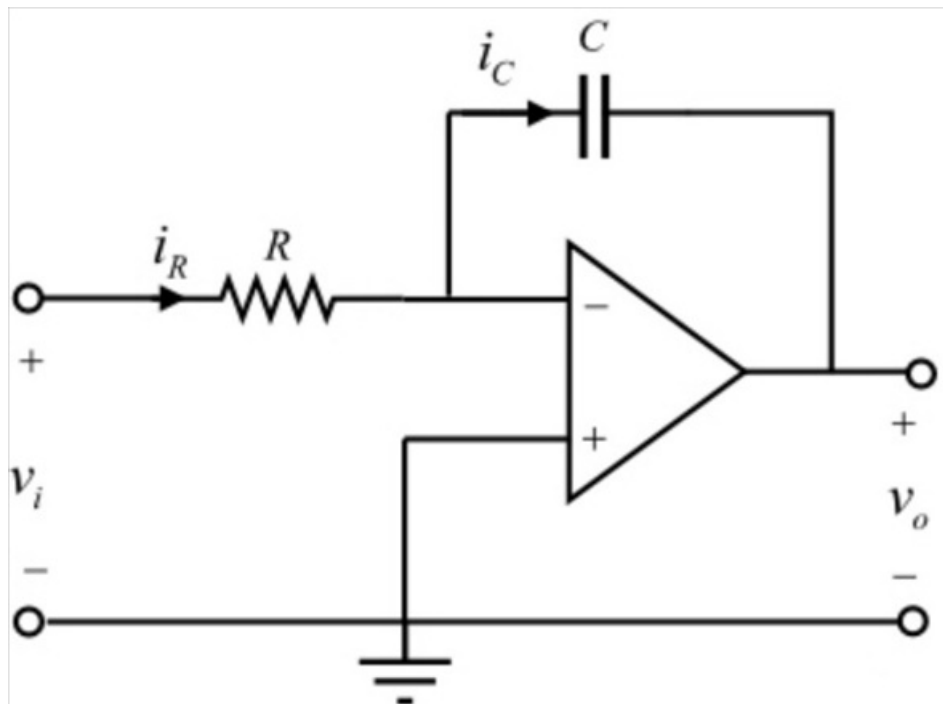


Figure 1

Step 2 of 3

Refer to equation 6.35 in the textbook.

Consider the expression for the output voltage of the integrator.

$$v_o = -\frac{1}{RC} \int_0^t v_i dt + v(0)$$

Substitute $50 \text{ k}\Omega$ for R , $100 \mu\text{F}$ for C and 6 V for v_i .

Assume the initial capacitor voltage is zero.

$$\begin{aligned} v_o &= -\frac{1}{(50 \times 10^3)(100 \times 10^{-6})} \int_0^t 6 dt + 0 \\ &= -\frac{1}{5} ([6t]_0^t) \\ &= -\frac{1}{5} (6t) \\ &= -1.2t \text{ V} \end{aligned}$$

$$v_o = -1.2t \text{ V}$$

Thus, the output voltage is $v_o = -1.2t \text{ V}$.

Step 3 of 3

Consider the Op-amp saturate at voltage $\pm 12 \text{ V}$.

$$v_o = \pm 12 \text{ V}$$

Therefore, on equating the output voltage with the saturation voltage,

$$-12 = -1.2t$$

$$t = \frac{12}{1.2}$$

$$t = 10 \text{ sec}$$

Therefore, the time taken by the op-amp to saturate at $\pm 12 \text{ V}$ is 10 seconds.