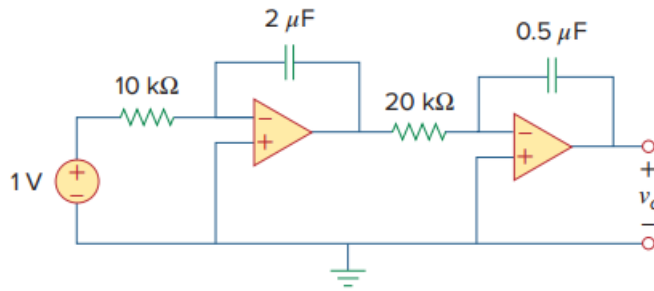


Problem

At $t = 1.5$ ms, calculate v_o due to the cascaded integrators in Fig. 6.89. Assume that the integrators are reset to 0 V at $t = 0$.

Fig. 6.89:



Step-by-step solution

Step 1 of 1

The output of the first Op- amp is

$$V_1 = \frac{-1}{RC} \int V_i dt$$

$$V_1 = -\frac{1}{10 \times 10^3 \times 2 \times 10^{-6}} \int_0^t V_i dt$$

$$V_1 = \frac{-100t}{2}$$

$$V_1 = -50t$$

$$V_o = \frac{-1}{RC} \int V_1 dt$$

$$V_o = -\frac{1}{20 \times 10^3 \times 0.5 \times 10^{-6}} \int_0^t (-50t) dt$$

$$V_o = 2500t^2$$

At $t = 1.5$ ms

$$V_o = 2500(1.5)^2 \times 10^{-6}$$

$$\therefore \boxed{V_o = 5.625 \text{ mV}}$$