

Chapter 6, Problem 82P

Problem

Design an op amp circuit such that

$$v_o = 10v_s + 2 \int v_s dt$$

where v_s and v_o are the input voltage and output voltage, respectively.

Step-by-step solution

Step 1 of 1

The circuit consists of a summer, an inverter and an integrator. Such circuit is shown below.

