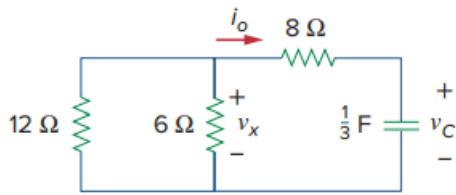


Problem

Refer to the circuit in Fig. 7.7. Let $v_C(0) = 60$ V. Determine v_C , v_x , and i_o for $t \geq 0$.

Fig. 7.7:



Step-by-step solution

Step 1 of 6

Consider the following circuit diagram:

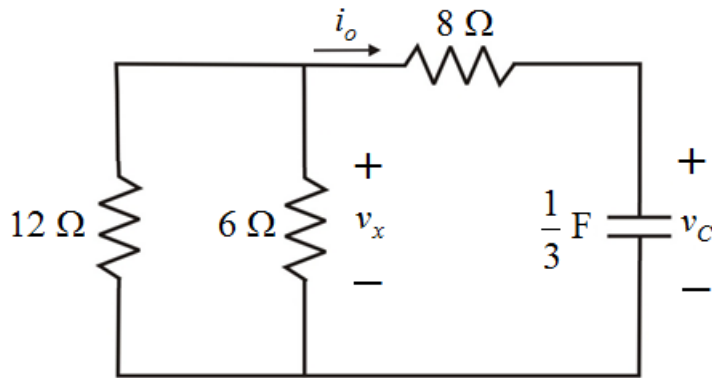


Figure 1

Step 2 of 6

Resistors $12\ \Omega$ and $6\ \Omega$ shown in Figure 1 are connected in parallel. Calculate an equivalent resistance of parallel resistors.

$$\begin{aligned} R &= \frac{(12)(6)}{12+6} \\ &= \frac{72}{18} \\ &= 4\ \Omega \end{aligned}$$

The parallel equivalent resistance is in series with $8\ \Omega$ resistor. Calculate the total equivalent resistance.

$$\begin{aligned} R_{eq} &= 4 + 8 \\ &= 12\ \Omega \end{aligned}$$

Step 3 of 6

Draw the modified circuit diagram after converting parallel series resistors into equivalent.

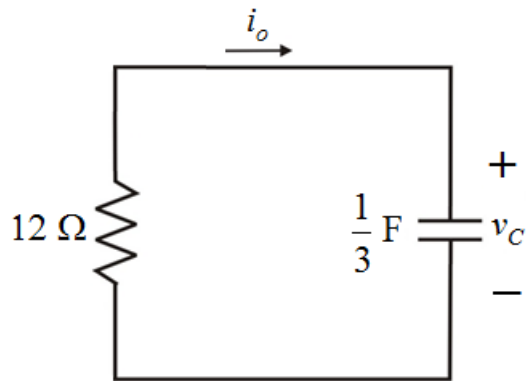


Figure 2

Step 4 of 6

Calculate the time constant.

$$\begin{aligned}\tau &= R_{eq} C \\ &= (12) \left(\frac{1}{3} \right) \\ &= 4\text{ s}\end{aligned}$$

Calculate the voltage across the capacitor for $t > 0$.

$$\begin{aligned}v_C(t) &= v_C(0) e^{-\frac{t}{\tau}} \\ &= (60) e^{-\frac{t}{4}} \\ &= 60e^{-0.25t}\text{ V}\end{aligned}$$

Therefore, the voltage across capacitor, $v_C(t)$ is $\boxed{60e^{-0.25t}\text{ V}}$.

Step 5 of 6

Apply Kirchhoff's current law at node v_x to the Figure 1.

$$\begin{aligned}\frac{v_x}{12} + \frac{v_x}{6} + \frac{v_x - v_C}{8} &= 0 \\ \left(\frac{1}{12} + \frac{1}{6} + \frac{1}{8} \right) v_x &= \frac{v_C}{8} \\ \left(\frac{2+4+3}{24} \right) v_x &= \frac{60e^{-0.25t}}{8} \\ v_x &= \frac{(24)(60e^{-0.25t})}{(8)(9)} \\ &= 20e^{-0.25t}\text{ V}\end{aligned}$$

Therefore, the voltage across resistor, v_x is $\boxed{20e^{-0.25t}\text{ V}}$.

Step 6 of 6

Calculate the current through $8\ \Omega$ resistor.

$$\begin{aligned} i_o(t) &= \frac{v_x(t) - v_c(t)}{8} \\ &= \frac{20e^{-0.25t} - 60e^{-0.25t}}{8} \\ &= -\frac{40}{8}e^{-0.25t} \\ &= -5e^{-0.25t}\text{ A} \end{aligned}$$

Therefore, the current through $8\ \Omega$ resistor, i_o is $\boxed{-5e^{-0.25t}\text{ A}}$.