

Chapter 7, Problem 1RQ

Problem

An RC circuit has $R = 2\ \Omega$ and $C = 4\ \text{F}$. The time constant is:

- (a) 0.5 s
- (b) 2 s
- (c) 4 s
- (d) 8 s
- (e) 15 s

Step-by-step solution

Step 1 of 1

Calculate the time constant for an RC circuit using the following formula.

$$\tau = RC$$

Substitute $2\ \Omega$ for resistance R and $4\ \text{F}$ for capacitance C .

$$\begin{aligned}\tau &= 4(2) \\ &= 8\ \text{s}\end{aligned}$$

Thus, the value of the time constant for an RC circuit is $8\ \text{s}$. Hence the correct option is **d**.

As the option d is correct remaining options are not suitable for the correct option.