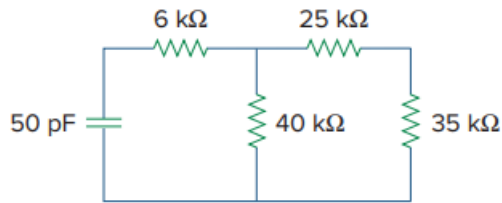


Problem

Determine the time constant for the circuit in Fig. 7.83.

Fig. 7.83:



Step-by-step solution

Step 1 of 4

The expression for the time constant of the circuit is,

$$\tau = R_{eq} C$$

Here R_{eq} is the equivalent resistance seen by the capacitor.

Consider the circuit in Figure 1 to calculate R_{eq} .

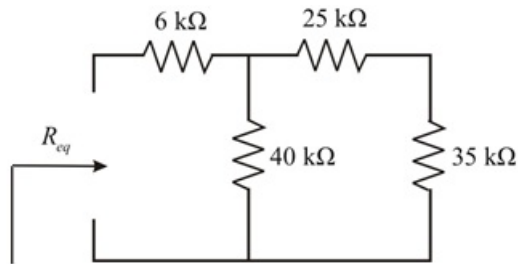


Figure 1

Step 2 of 4

From Figure 1, $25\text{ k}\Omega$ and $35\text{ k}\Omega$ resistors are in series. Hence the equivalent resistance is,

$$\begin{aligned} R_{eq1} &= 25\text{ k}\Omega + 35\text{ k}\Omega \\ &= 60\text{ k}\Omega \end{aligned}$$

The circuit is reduced to as shown in Figure 2.

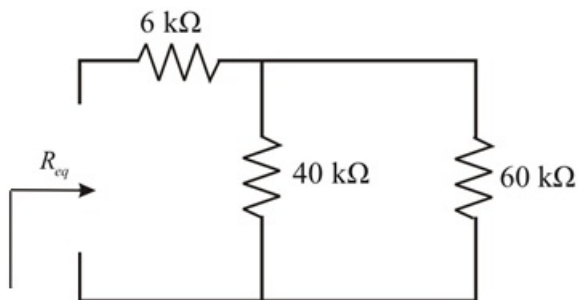


Figure 2

Step 3 of 4

From Figure 2, $60\text{ k}\Omega$ and $40\text{ k}\Omega$ are in parallel.

Hence,

$$\begin{aligned} R_{eq2} &= \frac{60\text{k} \times 40\text{k}}{60\text{k} + 40\text{k}} \\ &= 24\text{ k}\Omega \end{aligned}$$

The circuit is reduced to as shown in Figure 3.

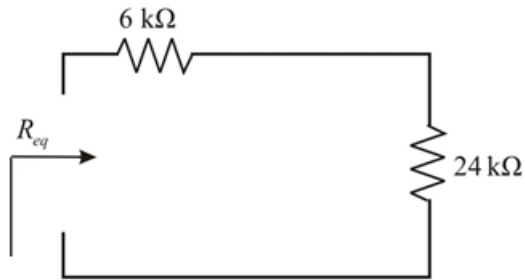


Figure 3

Step 4 of 4

From Figure 3, the $6\text{ k}\Omega$ and $24\text{ k}\Omega$ resistors are in parallel. Hence the equivalent resistance seen by the capacitor is,

$$\begin{aligned} R_{eq} &= 24\text{ k}\Omega + 6\text{ k}\Omega \\ &= 30\text{ k}\Omega \end{aligned}$$

The time constant of the circuit is,

$$\tau = R_{eq} C$$

Substitute $30\text{ k}\Omega$ for R_{eq} and 50 pF for C .

$$\begin{aligned} \tau &= (50 \times 10^{-12}) (30 \times 10^3) \\ &= 1.5 \times 10^{-6} \\ &= 1.5\text{ }\mu\text{sec} \end{aligned}$$

Thus, the time constant of the circuit is $1.5\text{ }\mu\text{sec}$.