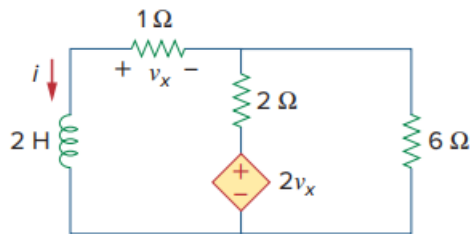


Problem

Find i and v_x in the circuit of Fig. 7.15. Let $i(0) = 7$ A.

Fig. 7.15:



Step-by-step solution

Step 1 of 5

Refer to Figure 7.15 in the textbook.

Redraw the circuit diagram with current notations as shown in Figure 1.

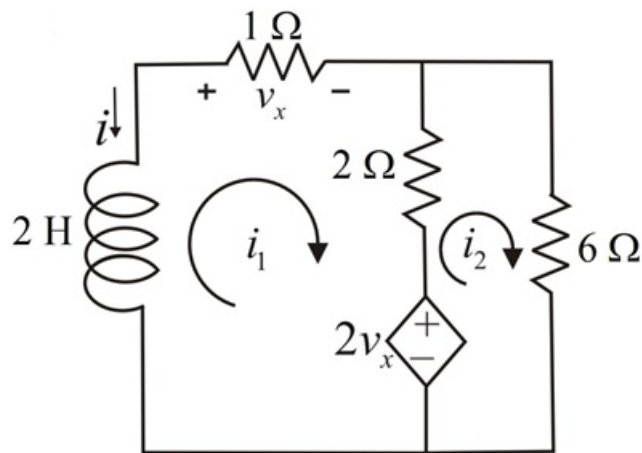


Figure 1

Step 2 of 5

Apply Kirchhoff's voltage law in loop 1.

$$2 \frac{di_1}{dt} + (1)i_1 + 2(i_1 - i_2) + 2v_x = 0$$

$$2 \frac{di_1}{dt} + 3i_1 - 2i_2 + 2v_x = 0 \quad \dots\dots (1)$$

Apply Kirchhoff's voltage law in loop 2.

$$-2v_x + 2(i_2 - i_1) + 6i_2 = 0$$

$$-2v_x + 8i_2 - 2i_1 = 0 \quad \dots\dots (2)$$

From circuit diagram in Figure 2, the voltage v_x is as follows:

$$\begin{aligned} v_x &= (1)i_1 \\ &= i_1 \quad \dots\dots (3) \end{aligned}$$

Step 3 of 5

Substitute i_1 for v_x in equation (1).

$$2 \frac{di_1}{dt} + 3i_1 - 2i_2 + 2i_1 = 0$$

$$2 \frac{di_1}{dt} + 5i_1 - 2i_2 = 0 \dots\dots (4)$$

Substitute i_1 for v_x in equation (2).

$$-2i_1 + 8i_2 - 2i_1 = 0$$

$$8i_2 - 4i_1 = 0$$

$$4i_1 = 8i_2$$

$$i_2 = \frac{i_1}{2} \dots\dots (5)$$

Step 4 of 5

Substitute $\frac{i_1}{2}$ for i_2 in the equation (4).

$$2 \frac{di_1}{dt} + 5i_1 - 2\left(\frac{i_1}{2}\right) = 0$$

$$2 \frac{di_1}{dt} + 5i_1 - i_1 = 0$$

$$2 \frac{di_1}{dt} + 4i_1 = 0$$

$$\frac{di_1}{dt} = -2i_1$$

$$\frac{di_1}{i_1} = -2dt \dots\dots (6)$$

Integrate equation (6) on both sides.

$$\int_{i(0)}^{i(t)} \frac{1}{i_1} di = -2 \int_0^t dt$$

$$\ln i_1 \Big|_{i(0)}^{i(t)} = -2t$$

$$\ln \frac{i_1(t)}{i_1(0)} = -2t$$

$$\frac{i_1(t)}{i_1(0)} = e^{-2t}$$

$$i_1(t) = i_1(0)e^{-2t}$$

Since $i(t) = -i_1(t)$, therefore,

$$[-i(t)] = [-i(0)]e^{-2t}$$

$$i(t) = i(0)e^{-2t}$$

Substitute 7 A for $i(0)$.

$$i(t) = 7e^{-2t} \text{ A}$$

Hence, the current through the inductor, $i(t)$ for $t > 0$ is $\boxed{7e^{-2t} \text{ A}}$.

Step 5 of 5

The voltage across the $1\ \Omega$ resistor is as follows:

$$\begin{aligned}v_x(t) &= -[i(t)](1) \\ &= -i(t)\end{aligned}$$

Substitute $7e^{-2t}$ A for $i(t)$.

$$v_x(t) = -7e^{-2t}\text{ V}$$

Hence, voltage across the $1\ \Omega$ resistor, $v_x(t)$ for $t > 0$ is $\boxed{-7e^{-2t}\text{ V}}$.