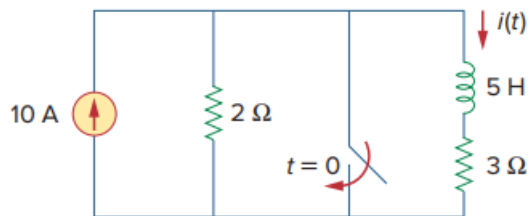


Problem

In the circuit of Fig. 7.80, $i(\infty)$ is:

- (a) 10 A
- (b) 6 A
- (c) 4 A
- (d) 2 A
- (e) 0 A

Fig. 7.80:



Step-by-step solution

Step 1 of 1

At $t = \infty$, the inductor current will be zero, i.e.,

$$i(\infty) = 0.$$