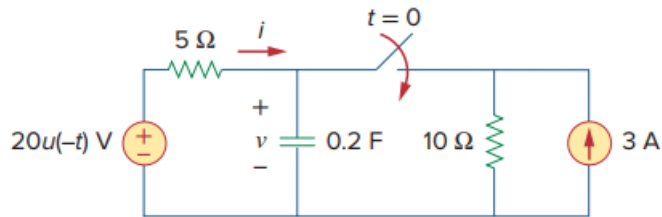


Problem

The switch in Fig. 7.47 is closed at $t = 0$. Find $i(t)$ and $v(t)$ for all time. Note that $u(-t) = 1$ for $t < 0$ and 0 for $t > 0$. Also, $u(-t) = 1 - u(t)$.


Fig. 7.47:



Step-by-step solution

Step 1 of 13

Given circuit diagram

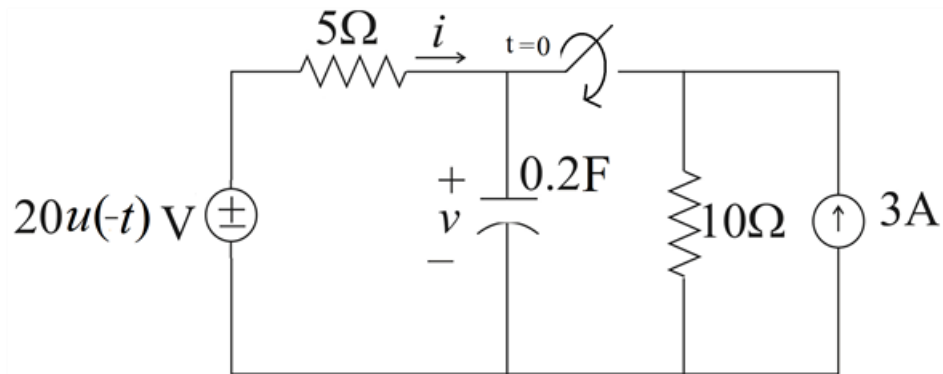

Step 2 of 13

The resistor current i is discontinuous at $t = 0$.

But capacitor voltage is continuous. Hence first find the capacitor voltage ' v '.


$$u(-t) = \begin{cases} 1 & t < 0 \\ 0 & t > 0 \end{cases}$$

Switch is closed at $t = 0$.

For $t < 0$ capacitor acts like an open circuit for dc.

Hence equivalent circuit for $t < 0$

Step 3 of 13

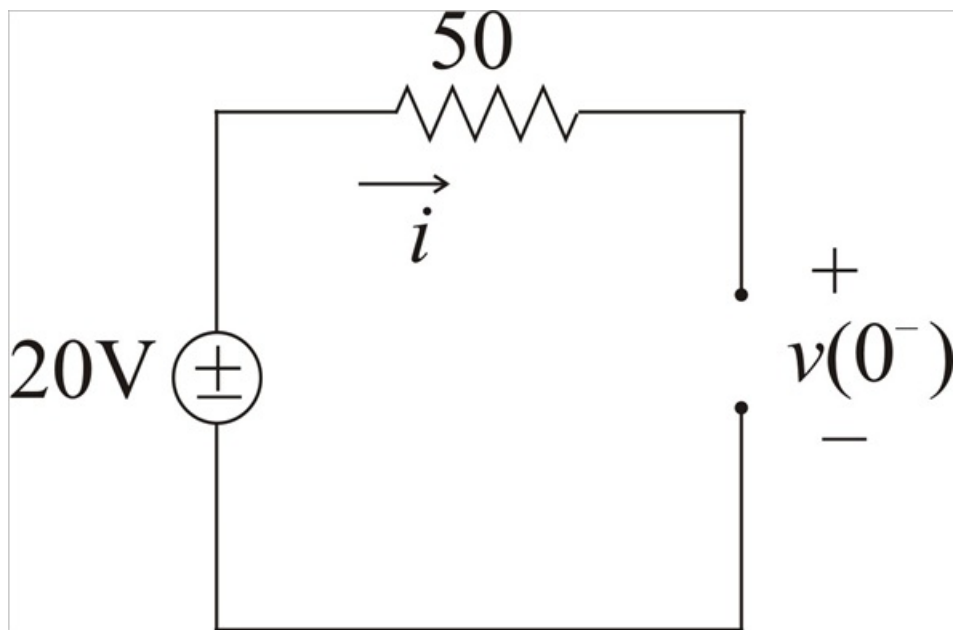

Step 4 of 13

From the above circuit $v_c(0^-) = 20\text{V}$


Capacitor voltage can't change instantaneously

$$v(0) = v(0^-) = v(0^+) = 20\text{V}$$

For $t < 0$, $i = 0$

Step 5 of 13

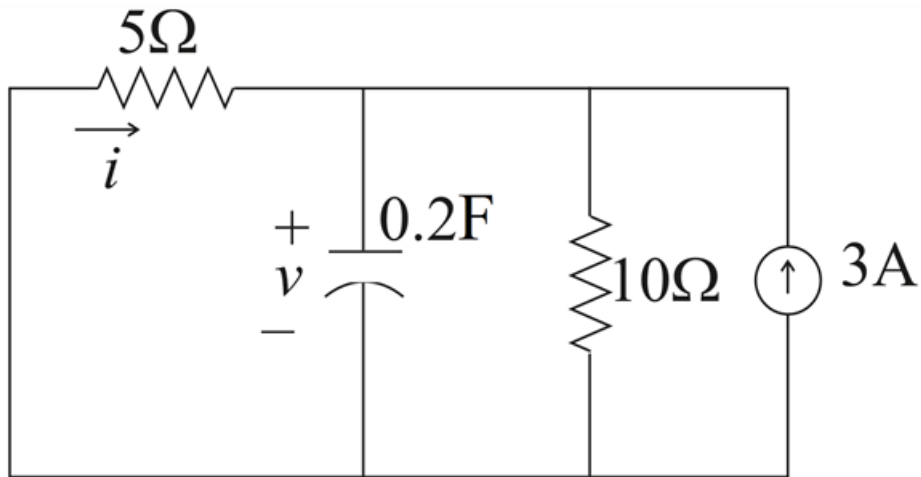For $t > 0$ switch is closed, equivalent circuit for the given circuit is as below




Step 6 of 13

After a long time, the circuit reaches steady state and the capacitor acts like an open circuit again.

Hence the circuit becomes as below

Step 7 of 13

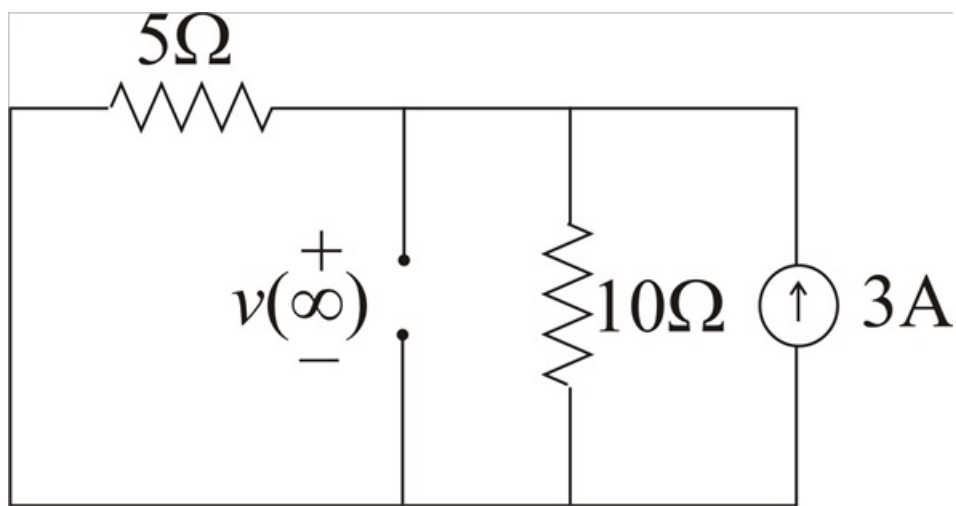

Step 8 of 13

By using current division rule we can write

$$I_{10\Omega} = 3 \times \frac{5}{5+10}$$


$$I_{10\Omega} = 1\text{ A}$$

$$\therefore v(\infty) = 10(I_{10\Omega})$$

$$v(\infty) = 10\text{ V}$$

Equivalent or Thevenin's resistance can be found by open circuiting current source and short circuiting voltage source

Step 9 of 13

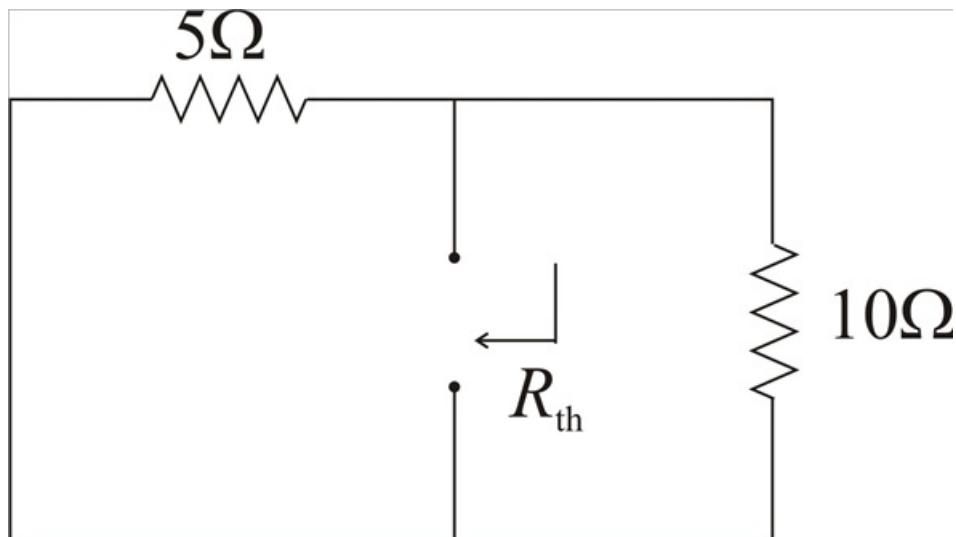

Step 10 of 13

$$R_{th} = 5 \parallel 10$$

$$R_{th} = \frac{5 \times 10}{10 + 5}$$

$$R_{th} = \frac{10}{3} \Omega$$

Step 11 of 13

Time constant $\tau = R_{th}C$

$$\tau = \frac{10}{3} \times 0.2$$

$$\tau = \frac{2}{3} \text{ sec}$$

Thus capacitor voltage is

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}$$

$$v(t) = 10 + (20 - 10)e^{-\frac{t}{\frac{2}{3}}} \text{ V for } t > 0$$

$$v(t) = 10 + 10e^{-\left(\frac{3}{2}\right)t} \text{ V for } t > 0$$

$$v(t) = 10(1 + e^{-1.5t}) \text{ V } t > 0$$

Step 12 of 13

For $t > 0$ applying KVL to left loop we can write

$$5i + v(t) = 0$$

$$i = -\frac{v(t)}{5}$$

$$i = \frac{-10(1 + e^{-1.5t})}{5}$$

$$i = -2(1 + e^{-1.5t}) \text{ A } t > 0$$

Step 13 of 13

Therefore $i(t)$ and $v(t)$ for all time

$$i(t) = \begin{cases} 0 \text{ A} & t < 0 \\ -2(1 + e^{-1.5t}) \text{ A} & t > 0 \end{cases}$$

$$v = \begin{cases} 20 \text{ V} & t < 0 \\ 10(1 + e^{-1.5t}) \text{ V} & t > 0 \end{cases}$$