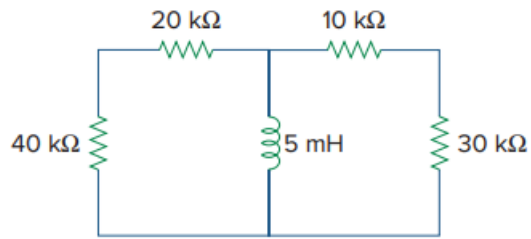


Problem

Calculate the time constant of the circuit in Fig. 7.94.

Fig. 7.94:



Step-by-step solution

Step 1 of 5

Consider the following circuit diagram:

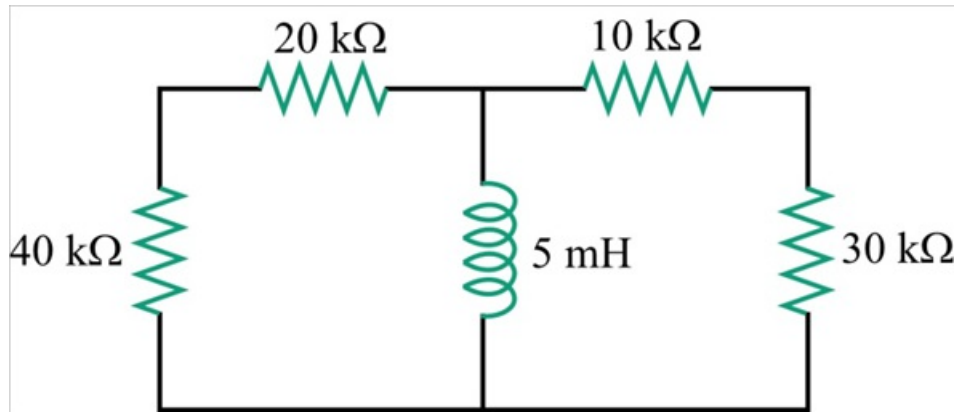


Figure 1

Step 2 of 5

Write the expression for time constant for LC circuit.

$$\tau = \frac{L}{R_{\text{eq}}}$$

Where,

L is the inductance

R_{eq} is the equivalent resistance

Step 3 of 5

Remove the inductor from the circuit shown in Figure 2, draw the modified circuit diagram:

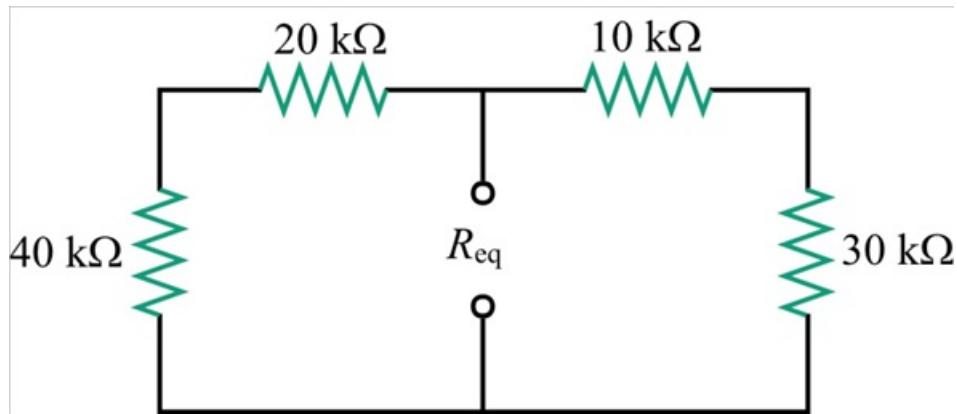


Figure 2

Step 4 of 5

Looking from the open terminals of the inductor, series connected $40\text{ k}\Omega$ and $20\text{ k}\Omega$ resistors are in parallel with series connected $40\text{ k}\Omega$ and $20\text{ k}\Omega$ resistors. Calculate the equivalent resistance.

$$\begin{aligned} R_{eq} &= (40\text{ k}\Omega + 20\text{ k}\Omega) \parallel (10\text{ k}\Omega + 30\text{ k}\Omega) \\ &= (60\text{ k}\Omega) \parallel (40\text{ k}\Omega) \\ &= \frac{(60\text{ k}\Omega)(40\text{ k}\Omega)}{60\text{ k}\Omega + 40\text{ k}\Omega} \\ &= \frac{2400\text{ k}\Omega}{100} \\ &= 24\text{ k}\Omega \end{aligned}$$

Step 5 of 5

Now calculate the time constant.

$$\begin{aligned} \tau &= \frac{L}{R_{eq}} \\ &= \frac{5\text{ mH}}{24\text{ k}\Omega} \\ &= 0.20833\text{ }\mu\text{s} \\ &= 208.33\text{ ns} \end{aligned}$$

Therefore, the time constant, τ is 208.33 ns.