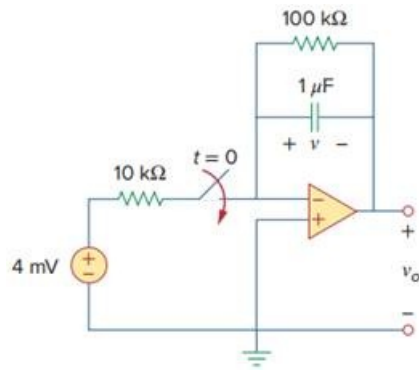


Problem

Find $v(t)$ and $v_o(t)$ in the op amp circuit of Fig. 7.58.

Fig. 7.58:



Step-by-step solution

Step 1 of 8

Refer to Figure 7.58 in the textbook.

Initially for $t < 0$, the switch is opened for long time and the capacitor acts as an open circuit as shown in Figure 1.

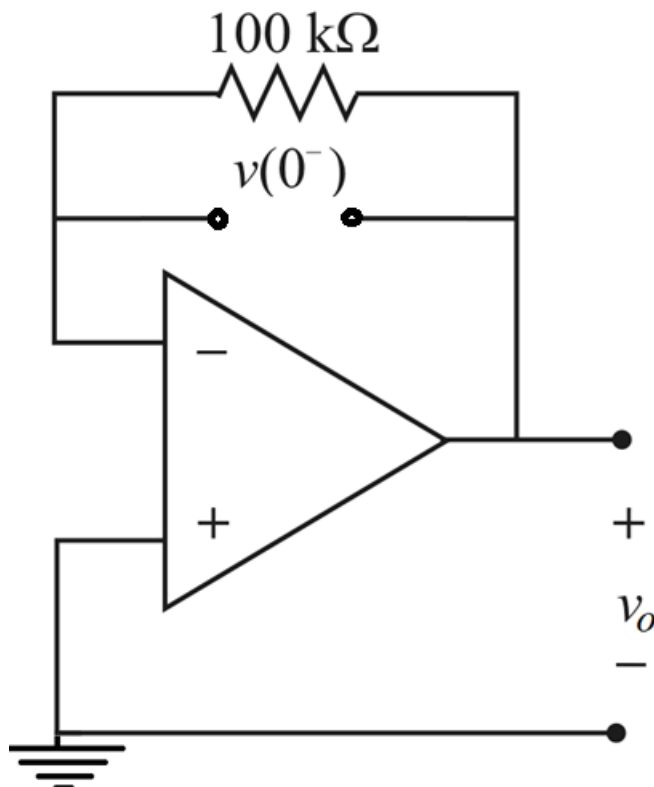


Figure 1

Step 2 of 8


Since it is a source free network, $v(0^-) = 0$.

Capacitor voltage can't change instantaneously. Therefore,

$$\begin{aligned} v(0) &= v(0^-) \\ &= v(0^+) \\ &= 0 \text{ V} \end{aligned}$$

Step 3 of 8

Draw the circuit diagram at $t = 0$.

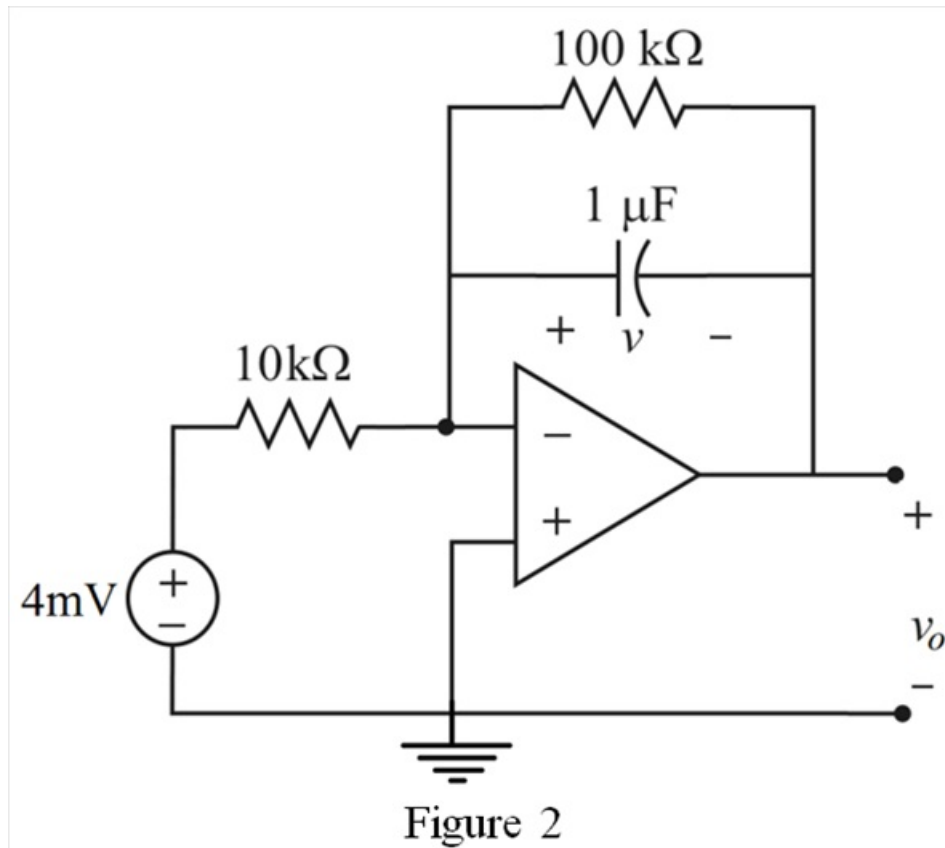

Step 4 of 8

From the virtual ground concept, the voltage at non-inverting terminal and inverting terminal is zero.

That is,

$$\begin{aligned} v_+ &= v_- \\ &= 0 \text{ V} \end{aligned}$$

Apply Kirchhoff's current law at inverting node.

$$\frac{0 - 4 \times 10^{-3}}{10 \times 10^3} + \frac{v}{100 \times 10^3} + 1 \times 10^{-6} \frac{dv}{dt} = 0$$

$$\frac{-4 \times 10^{-3}}{10 \times 10^3} + \frac{v}{100 \times 10^3} + 1 \times 10^{-6} \frac{dv}{dt} = 0$$

$$-4 \times 10^{-7} + 10^{-5} v + 10^{-6} \frac{dv}{dt} = 0$$

$$\frac{dv}{dt} + 10 v = 0.4 \dots\dots (1)$$

Step 5 of 8

The solution to the differential equation is,

$$v(t) = A + Be^{-\frac{t}{\tau}} \dots\dots (2)$$

Differentiate the equation (2) with respect to t .

$$\frac{dv(t)}{dt} = \frac{d}{dt} \left[A + Be^{-\frac{t}{\tau}} \right]$$

$$\frac{dv(t)}{dt} = -\frac{B}{\tau} e^{-\frac{t}{\tau}}$$

Step 6 of 8

Substitute $-\frac{B}{\tau} e^{-\frac{t}{\tau}}$ for $\frac{dv(t)}{dt}$ and $A + Be^{-\frac{t}{\tau}}$ for $v(t)$ in equation (1).

$$-\frac{B}{\tau} e^{-\frac{t}{\tau}} + 10 \left[A + Be^{-\frac{t}{\tau}} \right] = 0.4$$

$$-\frac{B}{\tau} e^{-\frac{t}{\tau}} + 10A + 10Be^{-\frac{t}{\tau}} = 0.4 \dots\dots (3)$$

Compare the constant terms in equation (3).

$$10A = 0.4$$

$$A = 0.04$$

Step 7 of 8

Substitute 0 for t in equation (1).

$$v(0) = A + Be^{-\frac{0}{\tau}}$$

$$0 = A + B$$

$$B = -0.04$$

Compare the exponential terms in equation (3).

$$10B - \frac{B}{\tau} = 0$$

$$10 = \frac{1}{\tau}$$

$$\tau = 0.1 \text{ sec}$$

Therefore, the expression for $v(t)$ is,

$$\begin{aligned} v(t) &= 0.04 - 0.04e^{-\frac{t}{0.1}} \text{ V} \\ &= 0.04 \left(1 - e^{-10t} \right) \text{ V} \\ &= 40 \left(1 - e^{-10t} \right) \text{ mV} \end{aligned}$$

Therefore, the expression for $v(t)$ is $\boxed{\begin{cases} 0 \text{ V} & \text{for } t < 0 \\ 40(1 - e^{-10t}) \text{ mV} & \text{for } t > 0 \end{cases}}$.

Step 8 of 8

From Figure 2,

$$V_- - v_o = v$$

$$0 - v_o = v$$

$$v_o = -v$$

$$= -40 \left(1 - e^{-10t} \right) \text{ mV}$$

$$= 40 \left(e^{-10t} - 1 \right) \text{ mV}$$

Therefore, the expression for $v_o(t)$ is $\boxed{\begin{cases} 0 \text{ V} & \text{for } t < 0 \\ 40(e^{-10t} - 1) \text{ mV} & \text{for } t > 0 \end{cases}}$.