

Problem

A circuit is described by

$$\frac{di}{dt} + 3i = 2u(t)$$

Find $i(t)$ for $t > 0$ given that $i(0) = 0$.

Step-by-step solution

Step 1 of 3

The differential equation of a circuit is,

$$\frac{di}{dt} + 3i = 2u(t)$$

$$\frac{di}{dt} = 2u(t) - 3i$$

$$\frac{di}{dt} = -(3i - 2)$$

$$\frac{di}{3i - 2} = -dt$$

Step 2 of 3

Apply integration on both sides.

$$\int_{i(0)}^{i(t)} \frac{di}{3i - 2} = - \int_0^t dt$$

$$\left[\frac{\ln(3i - 2)}{3} \right]_{i(0)}^{i(t)} = -[t]_0^t$$

$$\frac{1}{3} \ln \left(\frac{3i(t) - 2}{3i(0) - 2} \right) = -t \dots\dots (1)$$

Step 3 of 3

Substitute 0 for $i(0)$ in equation (1).

$$\ln\left(\frac{3i(t)-2}{3(0)-2}\right) = -3t$$

$$\ln\left(\frac{3i(t)-2}{-2}\right) = -3t$$

$$\frac{3i(t)-2}{-2} = e^{-3t}$$

$$3i(t)-2 = -2e^{-3t}$$

$$3i(t) = 2 - 2e^{-3t}$$

$$i(t) = \frac{2}{3} - \frac{2}{3}e^{-3t}$$

$$i(t) = \frac{2}{3}(1 - e^{-3t}) \text{ A}$$

Therefore, the expression for $i(t)$ is $\boxed{\frac{2}{3}(1 - e^{-3t}) \text{ A}}$.