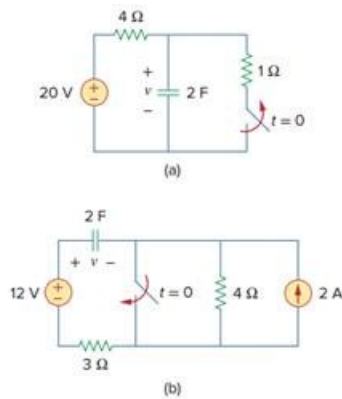


Problem

Calculate the capacitor voltage for $t < 0$ and $t > 0$ for each of the circuits in Fig. 7.106.


Fig. 7.106:



Step-by-step solution

Step 1 of 7

(a)

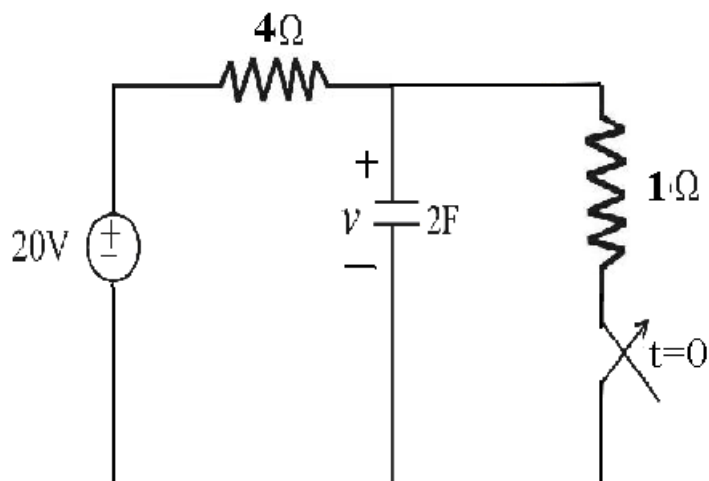

Step 2 of 7

(i)

For $t < 0$, the circuit is in steady state condition, so capacitor is replaced by open circuit

So,

$$v_C(0) = 20 \times \left(\frac{1}{1+4} \right)$$

$$v_C(0) = 20 \times \frac{1}{5}$$

$$\boxed{v_C(0) = 4V}$$

Step 3 of 7

(ii)

For $t > 0$, we have

$$v_C(t) = A - (A - B)e^{\frac{-t}{\tau}}$$

Where,

$$A = v_C(t \rightarrow \infty) \quad [\because C \text{ is open}]$$

$$\therefore A = 20 \text{ V}$$

$$B = v_C(t \rightarrow 0^+)$$

$$= v_C(t \rightarrow 0^-)$$

$$\therefore B = 4 \text{ V}$$

Step 4 of 7

Time constant,

$$\tau = R_{eq} C$$

$$\tau = (4) \times (2)$$


$$\therefore \tau = 8 \text{ s}$$

So, $v_C(t) = 20 - (20 - 4)e^{\frac{-t}{8}} \text{ V}$

$$\therefore v_C(t) = 20 - 16 e^{\frac{-t}{8}} \text{ V}$$

Step 5 of 7

(b)

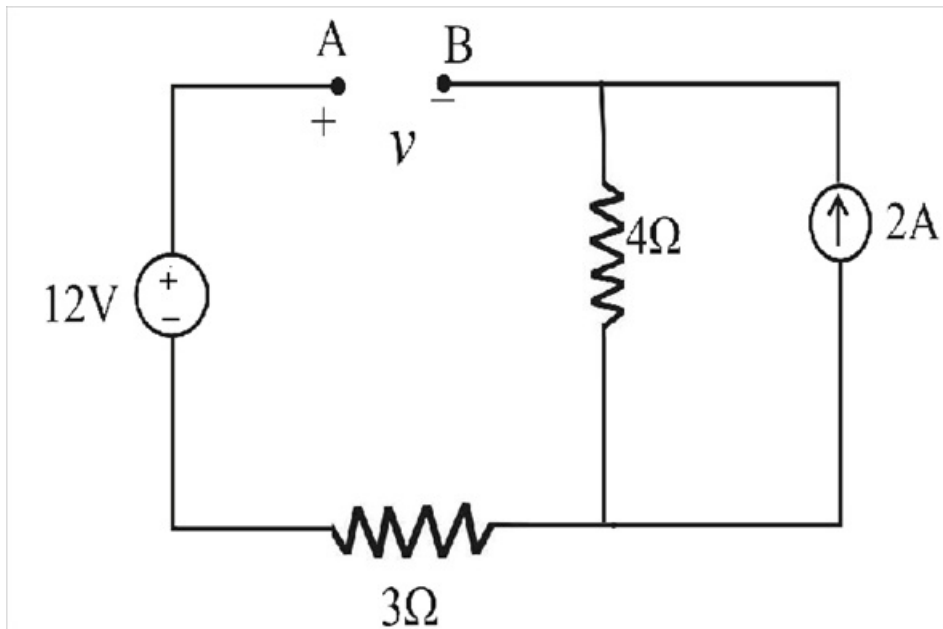

Step 6 of 7

(i)

For $t < 0$, steady state condition the capacitor is open circuited,

$V_C(0^-)$ is given by

$$v_A = 12 \text{ V}$$

$$v_B = 2 \times 4$$

$$\therefore v_B = 8 \text{ V}$$

So,

$$v_C = v_A - v_B$$

$$\therefore \boxed{v_C(0) = 4 \text{ V}}$$

(ii)

For $t > 0$ abrupt change ; so response is,

$$v_C(t) = A - (A - B)e^{\frac{-t}{\tau}}$$

$$A = v_C(t \rightarrow \infty)$$

$$A = 12 \text{ V}$$

$$B = v_C(t \rightarrow 0^+)$$

$$v_C(t \rightarrow 0^-) = 4 \text{ V}$$

$$\therefore B = 4 \text{ V}$$

Step 7 of 7

Time constant,

$$\tau = R_{eq} C$$

$$\tau = 3 \times 2$$

$$\therefore \tau = 6 \text{ s}$$

$$\therefore \boxed{v_C(t) = 12 - 8 e^{\frac{-t}{6}} \text{ V}}$$