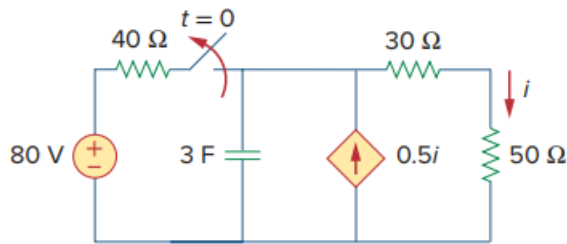


Problem

Consider the circuit in Fig. 7.110. Find $i(t)$ for $t < 0$ and $t > 0$.

Fig. 7.110:



Step-by-step solution

Step 1 of 12

Refer to Figure 7.110 in the textbook.

At $t = 0^-$, the circuit is at steady state. The capacitor acts as open circuit.

Draw the circuit diagram at $t = 0^-$.

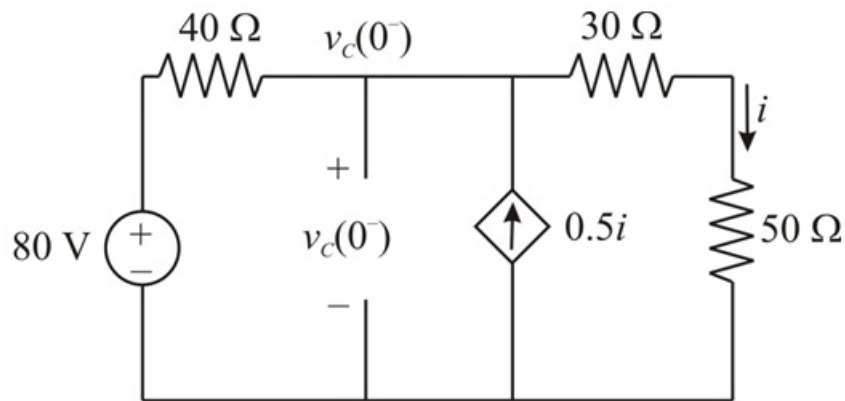


Figure 1

Step 2 of 12

Apply Ohm's law for the current through 50Ω resistor.

$$i = \frac{v_c(0^-)}{30 + 50}$$

$$= \frac{v_c(0^-)}{80}$$

Apply Kirchhoff's current law at node $v_c(0^-)$.

$$\frac{v_c(0^-) - 80}{40} - 0.5i + i = 0$$

$$\frac{v_c(0^-) - 80}{40} + 0.5i = 0$$

Step 3 of 12

Substituting $\frac{v_c(0^-)}{80}$ for i .

$$\frac{v_c(0^-) - 80}{40} + 0.5 \left[\frac{v_c(0^-)}{80} \right] = 0$$

$$\frac{2[v_c(0^-) - 80] + 0.5v_c(0^-)}{80} = 0$$

$$2v_c(0^-) - 160 + 0.5v_c(0^-) = 0$$

$$2.5v_c(0^-) = 160$$

$$v_c(0^-) = \frac{160}{2.5}$$

$$= 64 \text{ V}$$

Step 4 of 12

The capacitor voltage cannot be changed instantaneously.

$$v_c(0^-) = v_c(0^+) = v_c(0) = 64 \text{ V}.$$

Calculate the current, i for $t < 0$.

$$i = \frac{v_c(0^-)}{80}$$

Substituting 64 V for $v_c(0^-)$.

$$i = \frac{64}{80}$$

$$= 0.8 \text{ A}$$

Thus, the current, i for $t < 0$ is 0.8 A.

Step 5 of 12

For $t > 0$, the switch is open. Draw the modified circuit diagram.

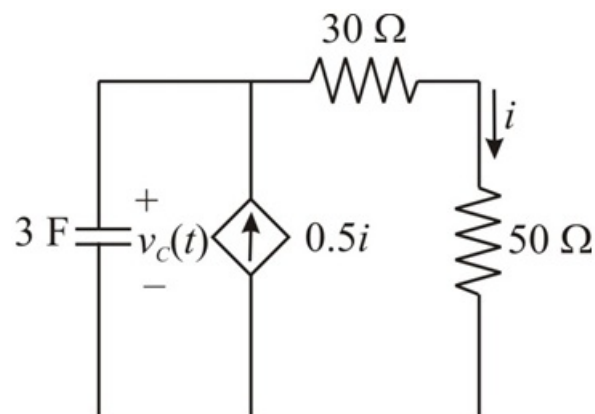


Figure 2

Step 6 of 12

At $t = \infty$, the circuit is at steady state and the capacitor behaves like an open circuit.

Draw the modified circuit diagram to calculate the final voltage across the capacitor.

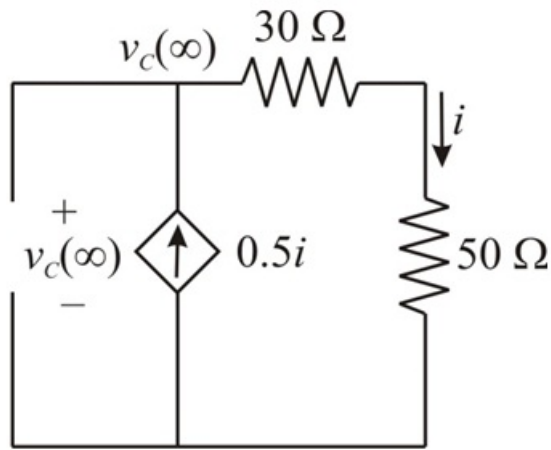


Figure 3

Step 7 of 12

The circuit is source free that is it does not have independent sources. So, the open circuited capacitor voltage is zero.

$$v_C(\infty) = 0 \text{ V}$$

Consider the expression for the capacitor voltage.

$$v_C(t) = v_C(\infty) + [v_C(0) - v_C(\infty)]e^{-\frac{t}{\tau}}$$

Here, the time constant is $\tau = R_{th}C$

Step 8 of 12

To calculate R_{th} , remove the capacitor and connect test current source and determine equivalent resistance.

Draw the modified circuit diagram.

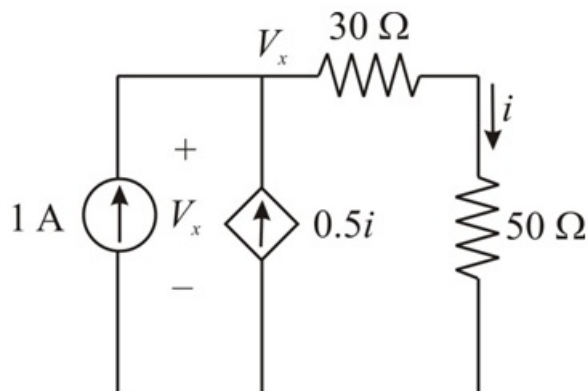


Figure 4

Step 9 of 12

Apply Ohm's law to calculate the expression for i .

$$i = \frac{V_x}{30 + 50}$$

$$= \frac{V_x}{80}$$

Apply Kirchhoff's current law at node V_x .

$$-1 - 0.5i + i = 0$$

$$-1 + 0.5i = 0$$

$$0.5i = 1$$

Substitute $\frac{V_x}{80}$ for i .

$$0.5 \left(\frac{V_x}{80} \right) = 1$$

$$V_x = 160$$

Step 10 of 12

Calculate the value of Thevenin's resistance, R_{Th} .

$$R_{Th} = \frac{V_x}{1 \text{ A}}$$

$$= \frac{160}{1}$$

$$= 160 \Omega$$

Calculate the value of time constant.

$$\tau = R_{Th} C$$

$$= (160)(3)$$

$$= 480 \text{ s}$$

Calculate the expression for capacitor voltage.

$$v_c(t) = v_c(\infty) + [v_c(0) - v_c(\infty)]e^{-\frac{t}{\tau}}$$

$$= 0 + (64 - 0)e^{-\frac{t}{480}}$$

$$= 64e^{-\frac{t}{480}} \text{ V}$$

Step 11 of 12

Draw the circuit for $t > 0$.

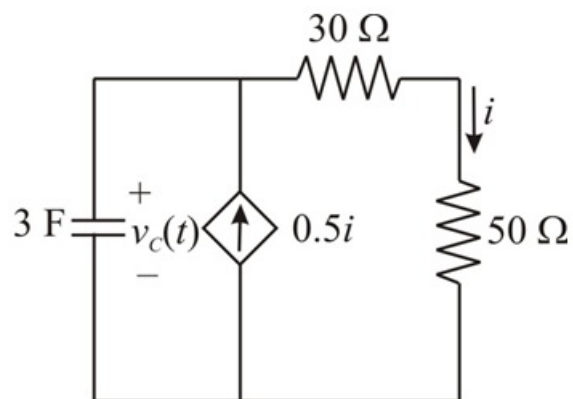


Figure 5

Step 12 of 12

Calculate the expression for the current, i .

$$\begin{aligned} i &= \frac{v_c(t)}{30 + 50} \\ &= \frac{v_c(t)}{80} \end{aligned}$$

Substituting $64e^{-\frac{t}{480}}$ V for $v_c(t)$.

$$\begin{aligned} i &= \frac{64e^{-\frac{t}{480}}}{80} \\ &= 0.8e^{-\frac{t}{480}} \text{ A} \end{aligned}$$

Thus, the current, i for $t > 0$ is $\boxed{0.8e^{-\frac{t}{480}} \text{ A}}$.