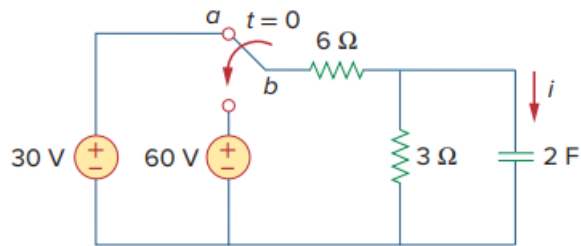


Problem

The switch in Fig. 7.111 has been in position *a* for a long time. At $t = 0$, it moves to position *b*. Calculate $i(t)$ for all $t > 0$.

Fig. 7.111:




Step-by-step solution

Step 1 of 8

Refer to figure 7.111 in the textbook.

Consider that the switch is moved to position 'b' at $t = 0$, before that it was in position 'a' for a long time. The capacitor acts like an open circuit in steady state condition.

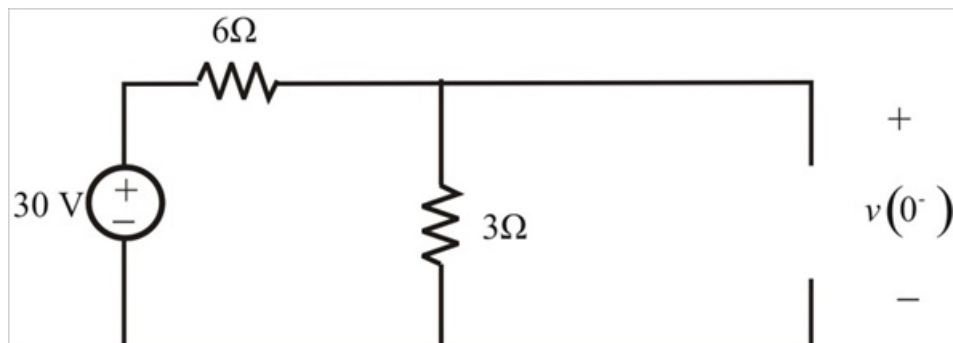Draw the circuit for $t = 0^-$ as shown in the following figure:



Step 2 of 8

Apply the voltage division rule. Therefore, the initial voltage across the capacitor is,


$$v(0^-) = 30 \times \frac{3}{6+3}$$

$$v(0^-) = 10 \text{ V}$$

Capacitor doesn't allow sudden changes in voltage.


$$v(0^-) = v(0^+) = v(0) = 10 \text{ V}$$

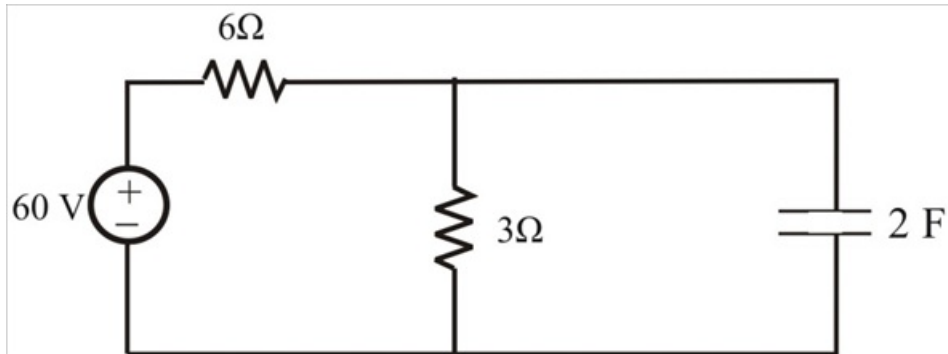Redraw the circuit for $t > 0$ as shown in the following figure:



Step 3 of 8

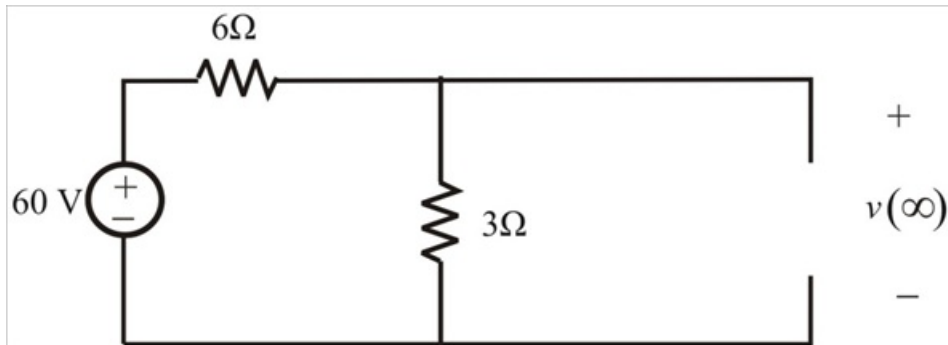Switch is in that position for a long time the circuit reached steady state and capacitor acts like an open circuit again. We obtained $v(\infty)$ by using voltage division rule



Step 4 of 8

The steady state voltage across the capacitor is,

$$v(\infty) = 60 \times \frac{3}{6+3}$$

$$v(\infty) = 20 \text{ V}$$

The expression for the voltage across the capacitor is,

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}$$

$$= 20 + [10 - 20]e^{-\frac{t}{\tau}}$$


$$v(t) = 20 - 10e^{-\frac{t}{\tau}} \text{ V}$$

Here, τ is time constant

$$\tau = R_{eq} C$$

Step 5 of 8

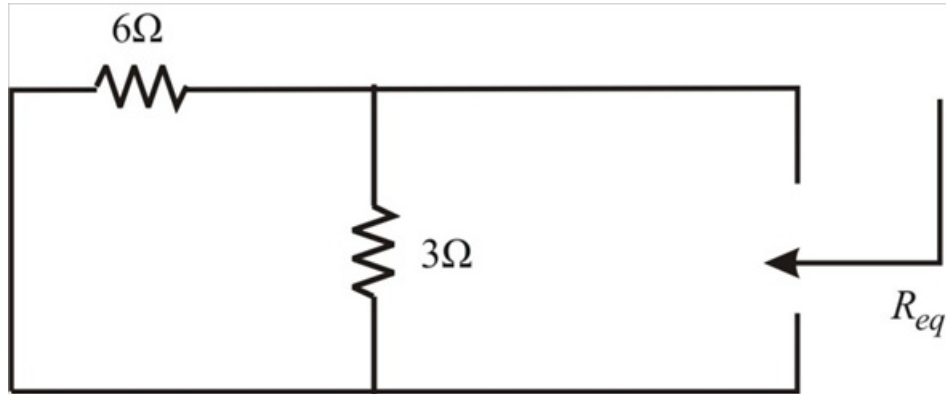Determine the equivalent resistance R_{eq} . Consider the following circuit:



Step 6 of 8

Calculate the equivalent resistance R_{eq} .

$$\begin{aligned} R_{eq} &= 3 \parallel 6 \\ &= \frac{3 \times 6}{3 + 6} \\ R_{eq} &= 2 \, \Omega \end{aligned}$$

Step 7 of 8

Calculate the time constant.

$$\begin{aligned} \tau &= 2 \times 2 \\ \tau &= 4 \text{ sec} \end{aligned}$$

Step 8 of 8

Therefore, the voltage across the capacitor is,

$$\begin{aligned} v(t) &= 20 - 10e^{-\frac{t}{4}} \text{ V} \\ v(t) &= 20 - 10e^{-0.25t} \text{ V} \end{aligned}$$

Therefore, the capacitor current is,

$$\begin{aligned} i(t) &= C \frac{dv(t)}{dt} \\ &= 2 \frac{d}{dt} (20 - 10e^{-0.25t}) \\ &= 2(-10)(-0.25e^{-0.25t}) \\ i(t) &= 5e^{-0.25t} \text{ A} \end{aligned}$$

Therefore, the value of current $i(t)$ for all $t > 0$ is $\boxed{5e^{-0.25t} \text{ A}}$.