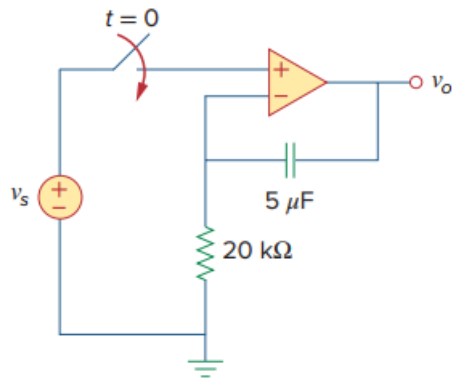


Problem

Determine v_o for $t > 0$ when $v_s = 20$ mV in the op amp circuit of Fig. 7.135.

Fig. 7.135:



Step-by-step solution


Step 1 of 4

Let V = Capacitor voltage.

For $t < 0$, Switch is open & $V(0) = 0$.

For $t > 0$, Switch is closed and the circuit becomes as shown below.

Step 2 of 4

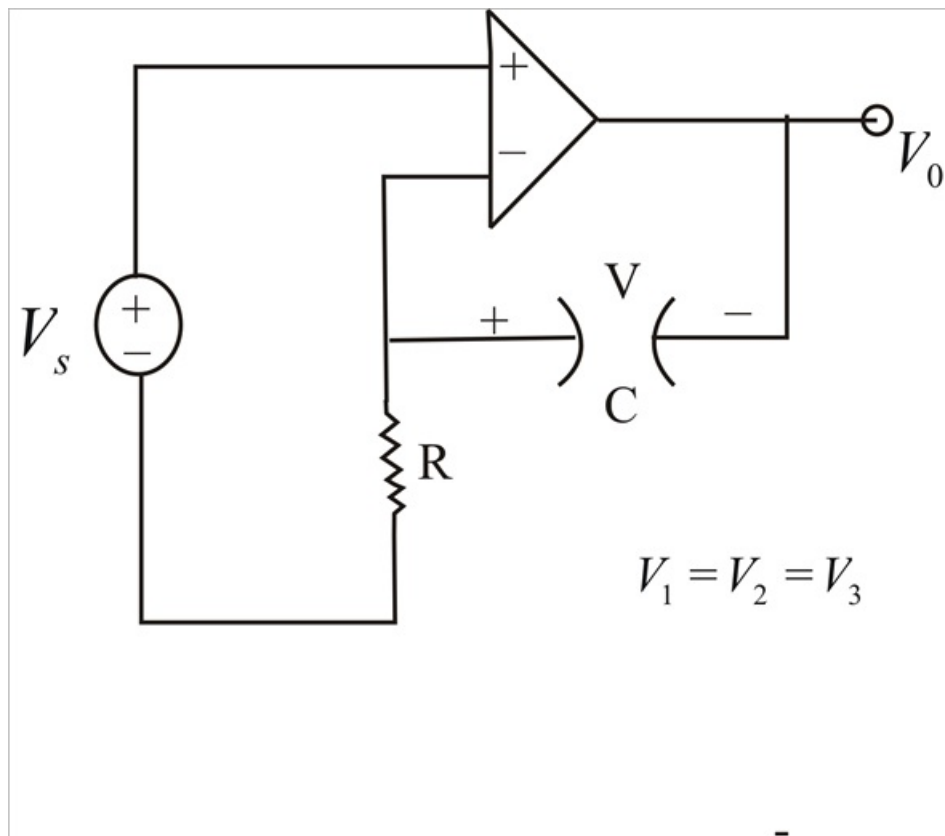

Step 3 of 4

$$V_1 = V_2 = V_s \rightarrow (1)$$

$$\frac{0-V_s}{R} = C \frac{dV}{dt} \rightarrow (2)$$

Where,

$$V = V_s - V_0 \Rightarrow V_0 = V_s - V \rightarrow (3)$$

From(1)

$$\frac{dV}{dt} + \frac{V_s}{R_C} = 0$$

$$V = -\frac{1}{R_C} \int V_s dt + V(0) = \frac{-tV_s}{R_C}$$

Step 4 of 4

Since V_s is constant.

$$R_C = (20 \times 10^3) (5 \times 10^{-6}) = 0.1$$

$$V = \frac{-20}{0.1} mV = -200t mV$$

From(3),

$$V_0 = V_s - V = 20 + 200t$$

$$= 20(1+10t) mV .$$