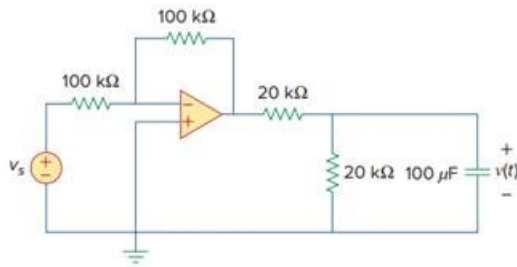


## Problem

For the op amp circuit in Fig. 7.136, suppose  $v_s = 10u(t)$  V. Find  $v(t)$  for  $t > 0$ .

Fig. 7.136:



## Step-by-step solution

## Step 1 of 7

Refer to Figure 7.136 in the textbook.

Draw the circuit diagram with notations.

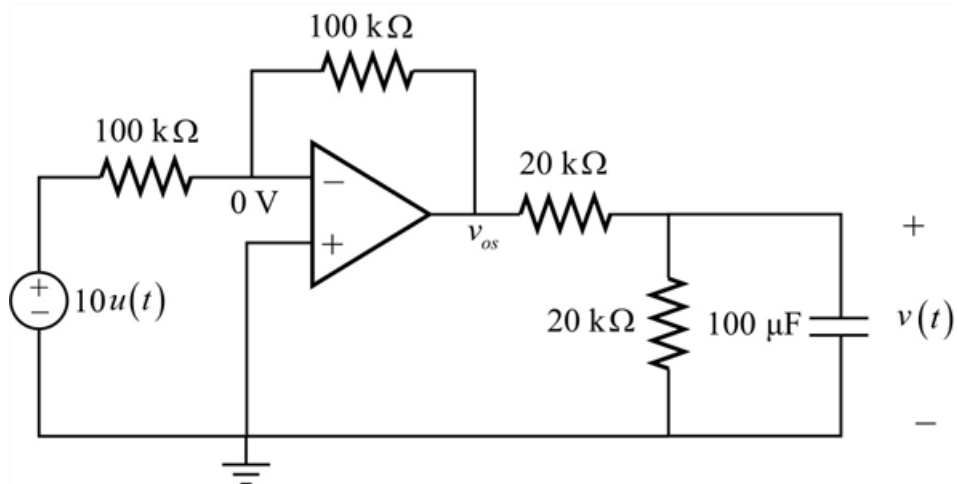


Figure 1

## Step 2 of 7

As per virtual ground concept, the voltage at the inverting terminal is equal the voltage at the non-inverting terminal.

$$v_p = v_n = 0 \text{ V}$$

Apply Kirchhoff's current law at the inverting terminal.

$$\frac{v_n - 10u(t)}{100 \text{ k}\Omega} + \frac{v_n - v_{os}}{100 \text{ k}\Omega} = 0$$

$$\frac{0 - 10u(t)}{100 \text{ k}\Omega} + \frac{0 - v_{os}}{100 \text{ k}\Omega} = 0$$


$$-10u(t) - v_{os} = 0$$

$$v_{os} = -10u(t) \text{ V}$$

## Step 3 of 7

Replace the output voltage of the op-amp with the voltage source.

Draw the modified circuit diagram.

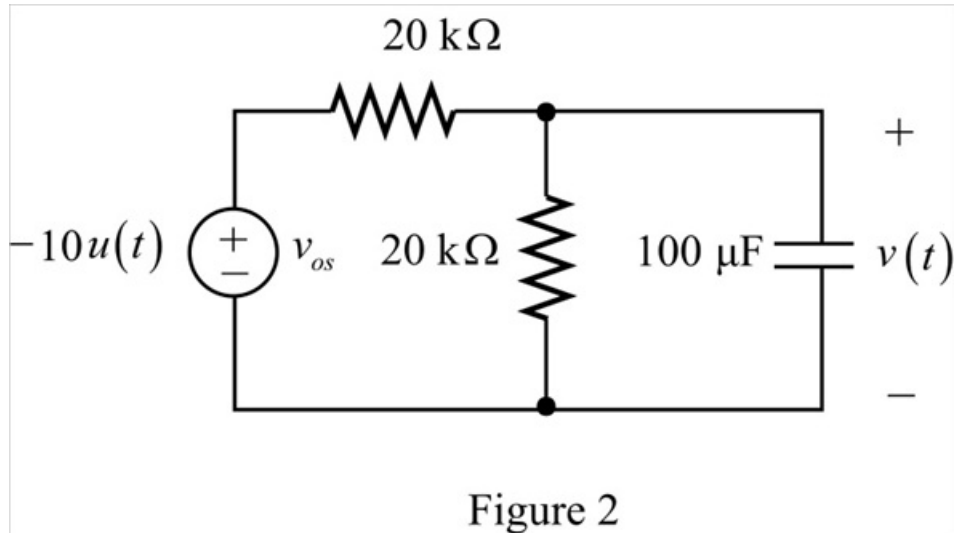

**Step 4** of 7


Consider the properties of step input.

$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$

The circuit is source free for  $t < 0$ , so the initial voltage across the capacitor is zero.

$$v(0) = 0\text{ V}$$

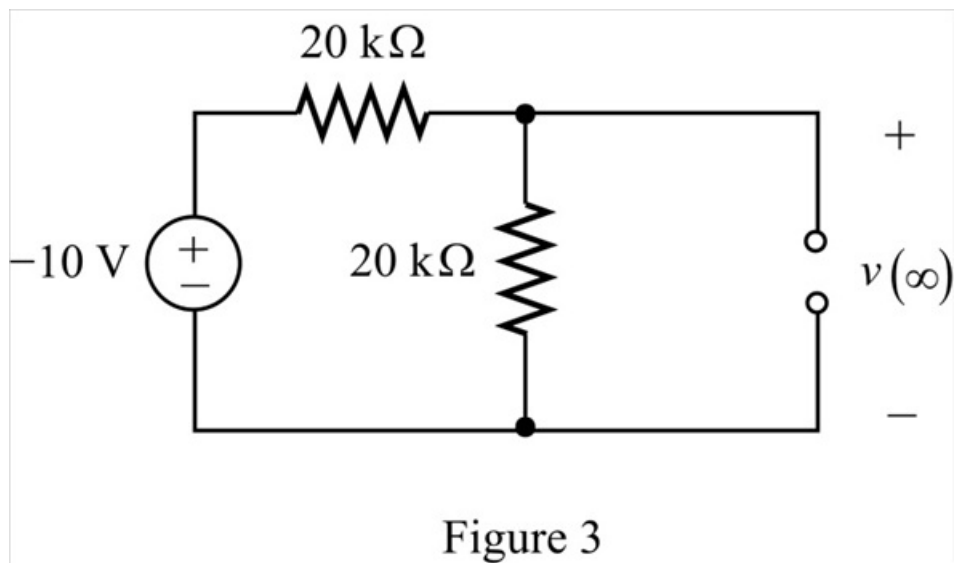Draw the circuit to calculate the final voltage across the capacitor.



**Step 5** of 7

Apply voltage division rule to calculate the final capacitor voltage.

$$\begin{aligned} v(\infty) &= \left( \frac{20 \text{ k}\Omega}{20 \text{ k}\Omega + 20 \text{ k}\Omega} \right) (-10) \\ &= \left( \frac{1}{2} \right) (-10) \\ &= -5 \text{ V} \end{aligned}$$

Draw the circuit to calculate the equivalent resistance for  $t > 0$ .

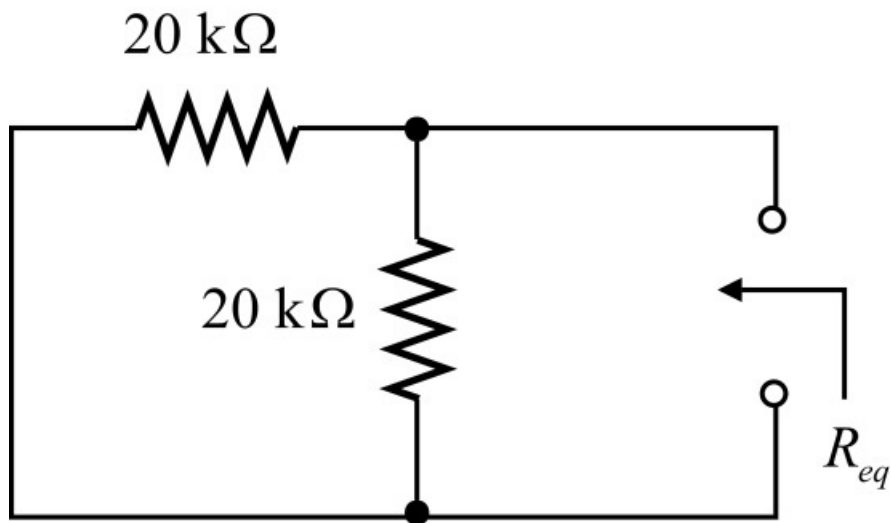


Figure 4

#### Step 6 of 7

The equivalent resistance for  $t > 0$  is,

$$\begin{aligned} R_{eq} &= 20 \text{ k}\Omega \parallel 20 \text{ k}\Omega \\ &= \frac{20 \times 20}{20 + 20} \text{ k}\Omega \\ &= 10 \text{ k}\Omega \end{aligned}$$

Calculate the value of time constant,  $\tau$ .

$$\tau = R_{eq} C$$

Substitute  $20 \text{ k}\Omega$  for  $R_{eq}$  and  $100 \mu\text{F}$  for  $C$ .

$$\begin{aligned} \tau &= (10 \times 10^3)(100 \times 10^{-6}) \\ &= 1 \text{ sec} \end{aligned}$$

#### Step 7 of 7

Calculate the expression for the capacitor voltage,  $v(t)$ .

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}$$

Substitute  $0 \text{ V}$  for  $v(0)$ ,  $-5 \text{ V}$  for  $v(\infty)$  and  $1 \text{ sec}$  for  $\tau$ .

$$\begin{aligned} v(t) &= -5 + (0 + 5)e^{-\frac{t}{1}} \\ &= (-5 + 5e^{-t})u(t) \text{ V} \end{aligned}$$

Thus, the expression for the capacitor voltage,  $v(t)$  is  $\boxed{(-5 + 5e^{-t})u(t) \text{ V}}$ .

