

Chapter 7, Problem 76P

Problem

Repeat Prob. 7.49 using *PSpice* or *MultiSim*.


Step-by-step solution

Step 1 of 3

The schematic is shown below. For the pulse, we use IPWL & enter the corresponding values as attributes as shown = 2 S. Since the W1 DM of the input pulse is 1S. After saving and simulating the circuit, we select

Trace/Add & Display -V(C1 : 2). The plot of V(t) is shown below.

Step 2 of 3

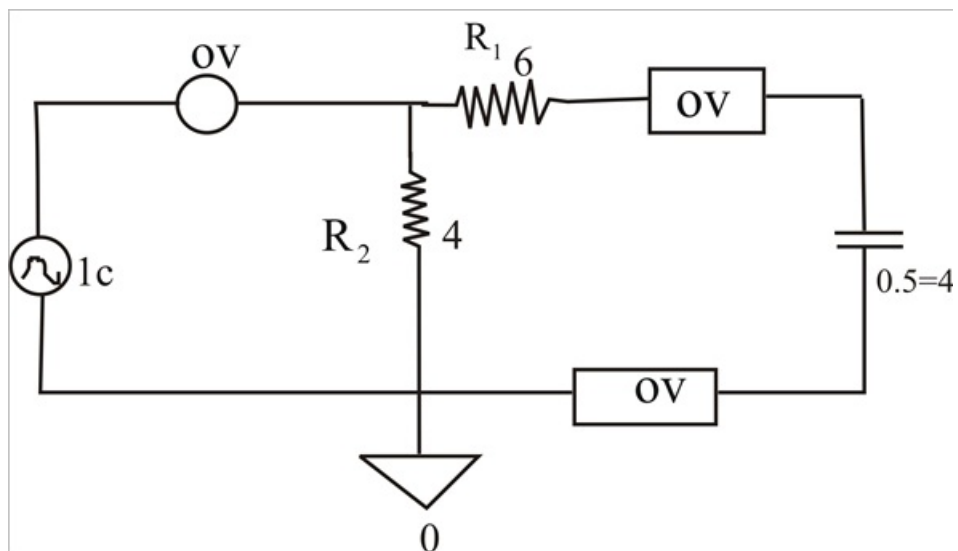

Step 3 of 3

