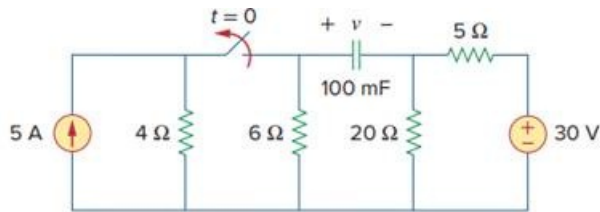


Problem

The switch in Fig. 7.141 opens at $t = 0$. Use *PSpice* or *MultiSim* to determine $v(t)$ for $t > 0$.

Fig. 7.141:



Step-by-step solution


Step 1 of 2

The schematic is shown below. We click, marker and insert mark voltage

Differential at the terminal of the capacitor to display V after simulation.

The plot of V is shown below.

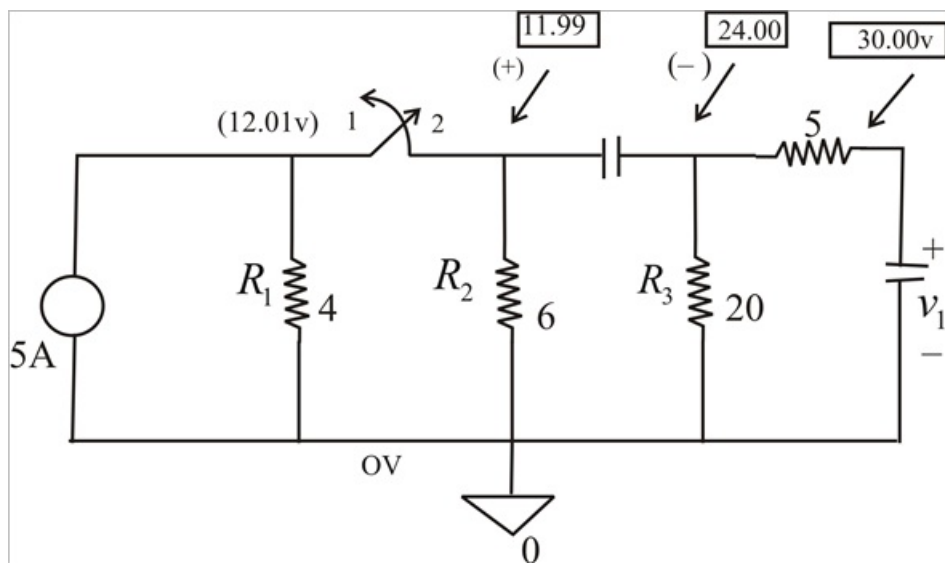Note from the plot that $V(0) = 12 \text{ V}$, $V(\infty) = -24 \text{ V}$ which are correct.



Step 2 of 2

