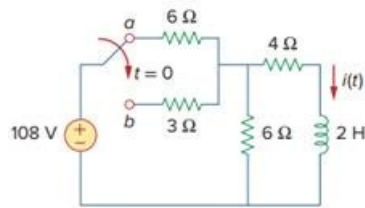


Problem

The switch in Fig. 7.142 moves from position *a* to *b* at $t = 0$. Use *PSpice* or *MultiSim* to find $i(t)$ for $t > 0$.

Fig. 7.142:



Step-by-step solution

Step 1 of 3


(A) When the switch is in position (a), Schematic is shown below.

We insert iprobe to display i , after simulation, we obtain,

$$i(0) = 7.714 \text{ A.}$$

From the display iprobe.

Step 2 of 3

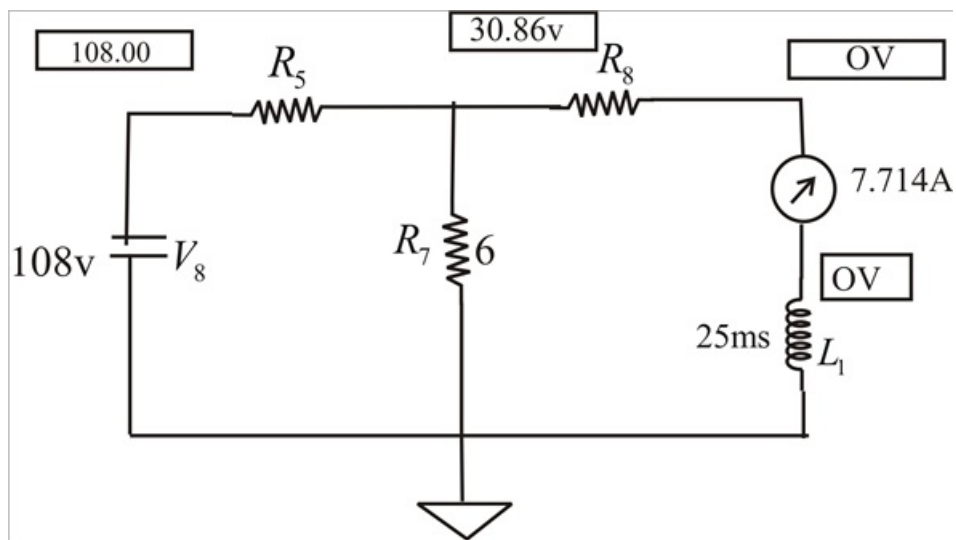

Step 3 of 3

(B) When the switch is in position (b), the schematic is as shown below. For Inductor L1, we let $L.C = 7.714$, by clicking Analysis/Setup/Transient. We let print setup print step = 25 m S.

Final step = 2 S.

After simulation, click Trace/Add in the probe menu & display $i(L1)$, as shown.

Note $i(\infty) = 12 \text{ A}$, which is correct.