

Problem

Repeat Prob. 7.65 using *PSpice* or *MultiSim*.


Step-by-step solution

Step 1 of 2

The schematic is shown below. We use VPWL, for the pulse and specify

The attributes as shown in the Analysis/Setup/Transient menu, we select

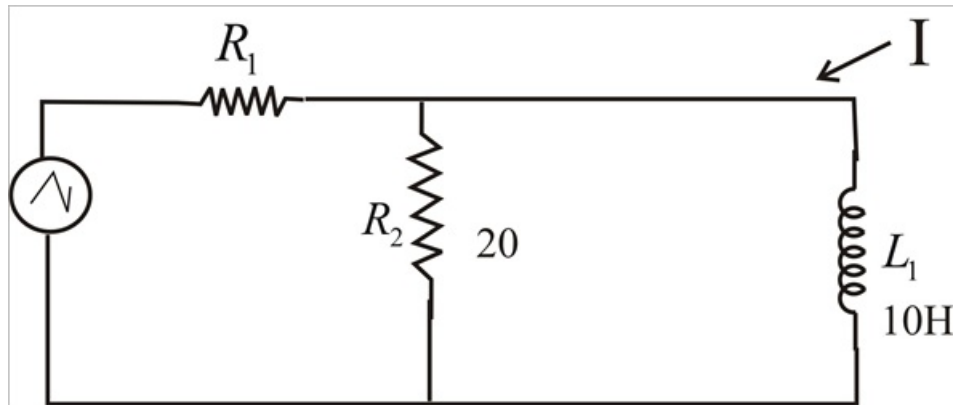Print setup = 25 ms, & Final setup = 35, by inserting a current, marker, at one terminal, Of 4, we automatically obtain the PWT of I after simulation as shown below.



Step 2 of 2

