

Problem

A capacitor with a value of 10 mF has a leakage resistance of 2 M Ω . How long does it take the voltage across the capacitor to decay to 40% of the initial voltage to which the capacitor is charged? Assume that the capacitor is charged and then set aside by itself.

Step-by-step solution

Step 1 of 4

Draw a circuit having capacitor with its leakage resistance.

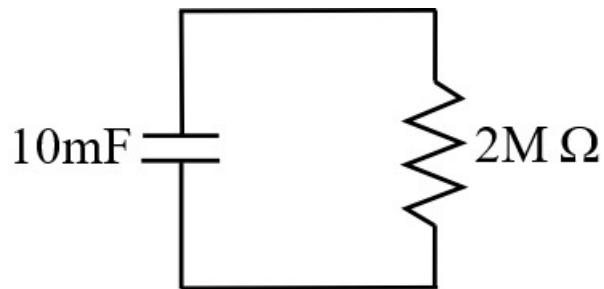


Figure 1

Step 2 of 4

The voltage across the capacitor is,

$$v_c(t) = v_c(\infty) + (v_c(0) - v_c(\infty))e^{\frac{-t}{\tau}} \dots\dots (1)$$

The final voltage across the capacitor $v_c(\infty)$ is,

$$v_c(\infty) = 0 \text{ V}$$

Then, rewrite the equation (1).

$$v_c(t) = (v_c(0))e^{\frac{-t}{\tau}} \dots\dots (2)$$

Step 3 of 4

The voltage across the capacitor decay to 40%. Then,

$$\begin{aligned} v_c(t) &= \frac{40}{100} v_c(0) \\ &= 0.4 v_c(0) \end{aligned}$$

Calculate the time constant τ .

$$\begin{aligned} \tau &= RC \\ &= 20 \times 10^3 \end{aligned}$$

Step 4 of 4

Substitute $0.4v_C(0)$ for $v_C(t)$ and 20×10^3 for τ in equation (2).

$$0.4v_C(0) = v_C(0)e^{-0.5 \times 10^{-3}t}$$

$$0.4 = e^{-0.5 \times 10^{-3}t}$$

Take the natural log.

$$0.4v_C(0) = v_C(0)e^{-0.5 \times 10^{-3}t}$$

$$0.4 = e^{-0.5 \times 10^{-3}t}$$

$$t = 1832 \text{ sec}$$

Hence, the capacitor takes 1832 sec to decay to 40% of the initial value.