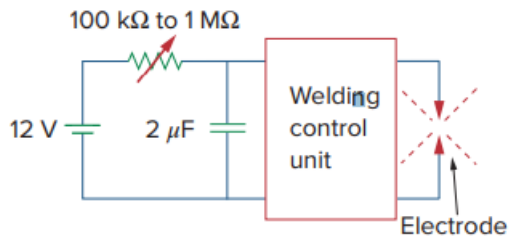


Problem

Figure 7.146 shows a circuit for setting the length of time voltage is applied to the electrodes of a welding machine. The time is taken as how long it takes the capacitor to charge from 0 to 8 V. What is the time range covered by the variable resistor?

Figure 7.146:



Step-by-step solution

Step 1 of 2

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-\frac{t}{\tau}}$$

$$V(\infty) = 12, V(0) = 0$$

$$V(t) = 12 \left[1 - e^{-\frac{t}{\tau}} \right]$$

$$V(t_0) = 8 = 12 \left[1 - e^{-\frac{t_0}{\tau}} \right]$$

$$\frac{8}{12} = 1 - e^{-\frac{t_0}{\tau}} \Rightarrow e^{-\frac{t_0}{\tau}} = \frac{1}{3}$$

$$t_0 = \tau \ln(3)$$

Step 2 of 2

For $R = 100 \text{ k}\Omega$

$$\tau = RC = (100 \times 10^3)(2 \times 10^{-6}) = 0.2 \text{ s}$$

$$t_0 = 0.2 \ln(3) = 0.2197 \text{ s}$$

Thus, Similarly where $R = 1 \text{ M}\Omega$, $t_0 = 2.197 \text{ s}$.

$$0.2197 \text{ s} < t_0 < 2.197 \text{ sec}$$

Thus,

$$0.2197 \text{ s} < t_0 < 2.197 \text{ sec.}$$