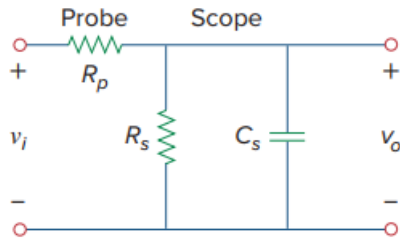


Problem

An attenuator probe employed with oscilloscopes was designed to reduce the magnitude of the input voltage v_i by a factor of 10. As shown in Fig. 7.149, the oscilloscope has internal resistance R_s and capacitance C_s , while the probe has an internal resistance R_p . If R_p is fixed at $6\text{ M}\Omega$, find R_s and C_s for the circuit to have a time constant of $15\text{ }\mu\text{s}$.

Fig. 7.149:




Step-by-step solution

Step 1 of 2

We determine the Thevenin's equivalent circuit for the capacitor C_s .
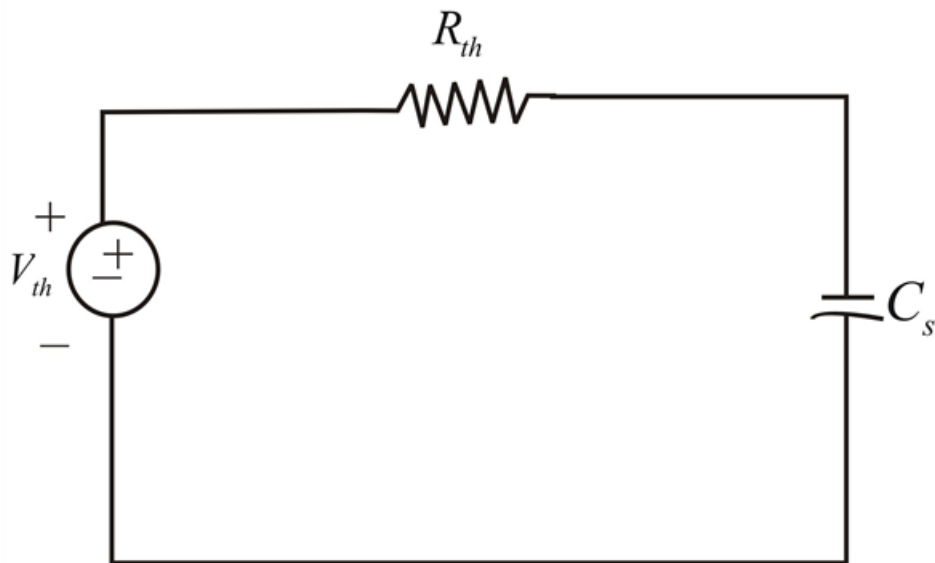
$$V_{th} = \frac{R_s}{R_s + R_p} V_i, \quad R_{th} = R_s \parallel R_p$$



Step 2 of 2

The Thevenin's equivalent is an RC circuit, Since,

$$V_{th} = \frac{1}{10}V_i \rightarrow \frac{1}{10} = \frac{R_s}{R_s + R_p}$$

$$R_s = \frac{1}{9}R_p = \frac{6}{9} = \frac{2}{3}M\Omega$$

Also,

$$\tau = R_{th}C_s = 15\mu S$$

Where,

$$R_{th} = R_p \parallel R_s = \frac{6(2/3)}{6 + 2/3} = 0.6M\Omega$$

$$C_s = \frac{\tau}{R_{th}} = \frac{15 \times 10^{-6}}{0.6 \times 10^6} = 25PF$$