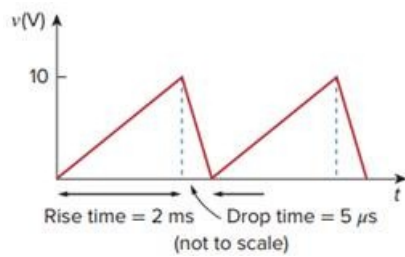


Problem

To move a spot of a cathode-ray tube across the screen requires a linear increase in the voltage across the deflection plates, as shown in Fig. 7.151. Given that the capacitance of the plates is 4 nF, sketch the current flowing through the plates.

Fig. 7.151:



Step-by-step solution

Step 1 of 2

$$i = C \frac{dV}{dt} = 4 \times 10^{-9} \begin{cases} \frac{10}{2 \times 10^{-3}} & 0 < t < t_r \\ \frac{-10}{5 \times 10^{-6}} & t_R < t < t_0 \end{cases}$$

$$i(t) = \begin{cases} 20 \mu A & 0 < t < 2 mS \\ -8 m A & 2 mS < t < 2 mS + 8 \mu S \end{cases}$$

Step 2 of 2

Which is sketched below

