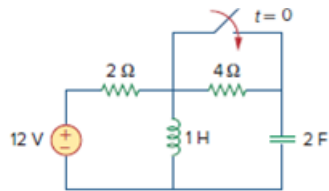


Problem

For the circuit in Fig. 8.58, the capacitor voltage at $t = 0^-$ (just before the switch is closed) is:

- (a) 0 V
- (b) 4 V
- (c) 8 V
- (d) 12 V

Figure 8.58:



Step-by-step solution

Step 1 of 1

At $t = 0^-$

$V_C = 0$ V