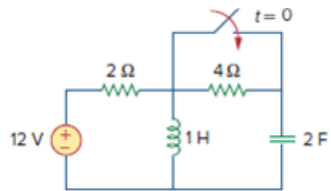


Problem

For the circuit in Fig. 8.58, the initial inductor current (at $t = 0$) is:

- (a) 0 A
- (b) 2 A
- (c) 6 A
- (d) 12 A

Figure 8.58:



Step-by-step solution

Step 1 of 1

At $t = 0$

Initial inductor current

$$i_L(0) = \frac{12V}{2\Omega} = 6A$$