

Chapter 8, Problem 6RQ

Problem

A parallel RLC circuit has $L = 2$ H and $C = 0.25$ F. The value of R that will produce a unity neper frequency is:

- (a) $0.5\ \Omega$
- (b) $1\ \Omega$
- (c) $2\ \Omega$
- (d) $4\ \Omega$

Step-by-step solution

Step 1 of 2

For a parallel RLC circuit,

Consider the expression for Neper frequency.

$$\alpha = \frac{1}{2RC} \dots\dots (1)$$

Step 2 of 2

Substitute 1 Np/s for α and 0.25 F for C .

$$1 = \frac{1}{2R(0.25)}$$

$$\begin{aligned} R &= \frac{1}{0.5} \\ &= 2\ \Omega \end{aligned}$$

Therefore, the required value of the resistance is $\boxed{2\ \Omega}$.