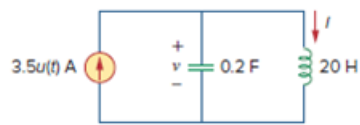


Problem

Find $i(t)$ and $v(t)$ for $t > 0$ in the circuit of Fig. 8.24.

Figure 8.24:



Step-by-step solution

Step 1 of 8

Refer to Figure 8.24 from the textbook.

Draw the modified circuit for $t < 0$.

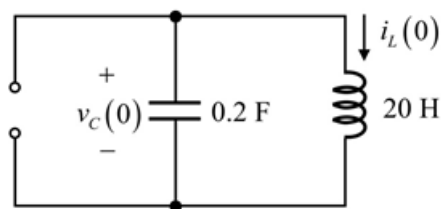


Figure 1

For $t < 0$, the step function, $u(t)$ is zero that is the current source $3.5u(t)$ is open circuit circuited. Hence the circuit becomes source free circuit.

Therefore, the initial values are,

$$i_L(0) = 0 \text{ A}$$

$$v_C(0) = 0 \text{ V}$$

Step 2 of 8

At $t = \infty$, as steady state is reached, capacitor is open circuited and inductor is short circuited.

Draw the modified circuit at $t = \infty$.

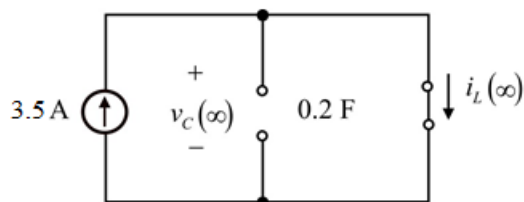


Figure 2

Calculate the steady state value of the current.

$$\begin{aligned} i_{ss}(t) &= i(\infty) \\ &= 3.5 \text{ A} \end{aligned}$$

Step 3 of 8

Draw the modified circuit for $t \geq 0$.

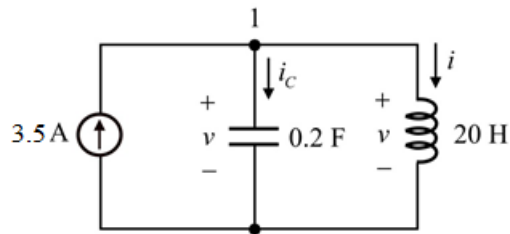


Figure 3

Step 4 of 8

For $t \geq 0$, the step function, $u(t)$ is one that is the current source $3.5u(t)$ is 3.5 A and the voltage across the inductor and capacitor is same because of the parallel circuit.

$$v = L \frac{di}{dt}$$

Apply Kirchhoff's current law at the node 1.

$$i_c + i = 3.5$$

$$C \frac{dv}{dt} + i = 3.5$$

Substitute $L \frac{di}{dt}$ for v .

$$C \frac{d}{dt} \left(L \frac{di}{dt} \right) + i = 3.5$$

$$LC \frac{d^2 i}{dt^2} + i = 3.5$$

$$\frac{d^2 i}{dt^2} + \frac{i}{LC} = \frac{3.5}{LC}$$

Step 5 of 8

Substitute 0.2 F for C and 20 H for L .

$$\frac{d^2 i}{dt^2} + \frac{i}{(0.2)(20)} = \frac{3.5}{(0.2)(20)}$$

$$\frac{d^2 i}{dt^2} + \frac{i}{4} = \frac{3.5}{4}$$

$$\frac{d^2 i}{dt^2} + 0.25i = 0.875$$

The associated polynomial is,

$$s^2 + 0.25 = 0$$

$$s = +j0.5, -j0.5$$

Step 6 of 8

Calculate the cut-off frequency, ω_0 .

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{(0.2)(20)}} \\ &= \frac{1}{\sqrt{4}} \\ &= 0.5\end{aligned}$$

Therefore, the expression for the current, $i(t)$ is,

$$\begin{aligned}i(t) &= i_{ss}(t) + i_t(t) \\ &= i_{ss}(t) + [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)] \\ &= 3.5 + [A_1 \cos(0.5t) + A_2 \sin(0.5t)]\end{aligned}$$

Substitute 0 for t .

$$\begin{aligned}i(0) &= 3.5 + [A_1 \cos 0.5(0) + A_2 \sin 0.5(0)] \\ 0 &= 3.5 + A_1 \\ A_1 &= -3.5\end{aligned}$$

Step 7 of 8

Differentiate the function $i(t)$ with respect to t .

$$\begin{aligned}\frac{di(t)}{dt} &= \frac{d}{dt} [3.5 + (A_1 \cos(0.5t) + A_2 \sin(0.5t))] \\ &= -A_1 \sin(0.5t) + A_2 \cos(0.5t)\end{aligned}$$

Substitute 0 for t .

$$\begin{aligned}\frac{di(0)}{dt} &= -A_1 \sin 0.5(0) + A_2 \cos 0.5(0) \\ 0 &= A_2 \\ A_2 &= 0\end{aligned}$$

Substitute 0 for A_2 and -3.5 for A_1 in $i(t)$.

$$\begin{aligned}i(t) &= 3.5 + [(-3.5) \cos(0.5t) + (0) \sin(0.5t)] \\ &= 3.5 - 3.5 \cos(0.5t) \\ &= 3.5 [1 - \cos(0.5t)]\end{aligned}$$

Therefore, the expression for the $i(t)$ for $t > 0$ is $\boxed{3.5 [1 - \cos(0.5t)] \text{ A}}$.

Step 8 of 8

Calculate the voltage, $v(t)$.

$$v(t) = L \frac{di(t)}{dt}$$

Substitute $3.5(1 - \cos 0.5t)$ for $i(t)$ and 20 H for L .

$$\begin{aligned} v(t) &= 20 \frac{d}{dt} [3.5(1 - \cos(0.5t))] \\ &= 70 \frac{d}{dt} [1 - \cos(0.5t)] \\ &= 70 [0 - 0.5(-\sin(0.5t))] \\ &= 35 \sin(0.5t) \end{aligned}$$

Therefore, the expression for the voltage, $v(t)$ is $\boxed{35 \sin(0.5t) \text{ A}}$.