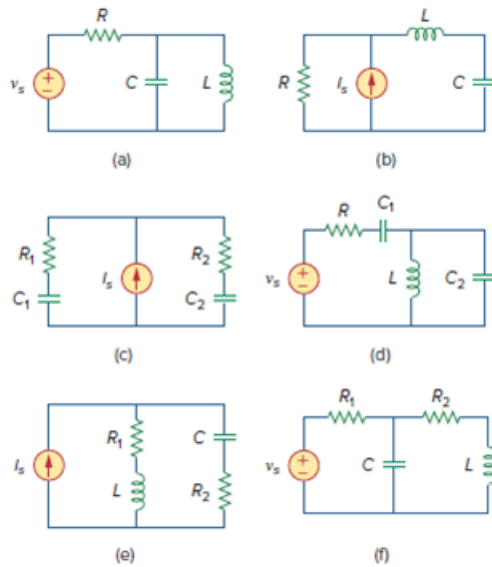


Problem

Match the circuits in Fig. 8.61 with the following items:

- (i) first-order circuit
- (ii) second-order series circuit
- (iii) second-order parallel circuit
- (iv) none of the above

Fig. 8.61:



Step-by-step solution

Step 1 of 6

(A) Second order parallel circuit (iii)

Step 2 of 6

(B) Second order series circuit (ii)

Step 3 of 6

(C) First order circuit (i)

Step 4 of 6

(D) (iv)

Step 5 of 6

(E) Second order series circuit (ii)

Step 6 of 6

(F) (iv)