

Problem

The differential equation that describes the current in an RLC network is

$$3 \frac{d^2 i}{dt^2} + 15 \frac{di}{dt} + 12i = 0$$

Given that $i(0) = 0$, $di(0)/dt = 6$ mA/s, obtain $i(t)$.

Step-by-step solution

Step 1 of 5

Consider the differential equation for the current.

$$3 \frac{d^2 i}{dt^2} + 15 \frac{di}{dt} + 12i = 0$$

$$\frac{d^2 i}{dt^2} + 5 \frac{di}{dt} + 4i = 0$$

Treat $\frac{d}{dt}$ as s .

$$s^2 i + 5s i + 4i = 0$$

$$(s^2 + 5s + 4)i = 0$$

Step 2 of 5

Consider the characteristic equation.

$$s^2 + 5s + 4 = 0$$

$$(s + 4)(s + 1) = 0$$

The roots of the characteristic equation are $s_1 = -4$ and $s_2 = -1$.

Step 3 of 5

The roots are negative and real. Hence, the equation exhibits the over damped response.

Consider the expression for the current $i(t)$.

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Substitute -4 for s_1 and -1 for s_2 .

$$i(t) = A_1 e^{-4t} + A_2 e^{-t} \dots\dots (1)$$

Substitute 0 for t .

$$i(0) = A_1 e^{-4(0)} + A_2 e^{-1(0)}$$

Substitute 0 for $i(0)$.

$$0 = A_1 e^{(0)} + A_2 e^{(0)}$$

$$0 = A_1 (1) + A_2 (1)$$

$$0 = A_1 + A_2$$

$$A_1 = -A_2$$

Step 4 of 5

Recall equation (1).

$$i(t) = A_1 e^{-4t} + A_2 e^{-1t}$$

Apply derivative with respect to t .

$$\begin{aligned}\frac{di(t)}{dt} &= A_1 \frac{de^{-4t}}{dt} + A_2 \frac{de^{-1t}}{dt} \\ &= -4A_1 e^{-4t} - 1A_2 e^{-1t}\end{aligned}$$

Substitute 0 for t .

$$\begin{aligned}\frac{di(0)}{dt} &= -4A_1 e^{-4(0)} - A_2 e^{-1(0)} \\ &= -4A_1 e^{(0)} - A_2 e^{(0)} \\ &= -4A_1 (1) - A_2 (1) \\ &= -4A_1 - A_2\end{aligned}$$

Substitute 6 mA/s for $\frac{di(0)}{dt}$ and $-A_2$ for A_1 .

$$6 \text{ m} = -4(-A_2) - A_2$$

$$6 \text{ m} = 4A_2 - A_2$$

$$3A_2 = 6 \text{ m}$$

$$A_2 = \frac{6 \text{ m}}{3}$$

$$A_2 = 2 \text{ m}$$

Therefore, the value of the constant A_2 is 2 m.

The value of the constant A_1 is -2 m since $A_1 = -A_2$.

Step 5 of 5

Recall equation (1).

$$i(t) = A_1 e^{-4t} + A_2 e^{-1t}$$

Substitute -2 m for A_1 and 2 m for A_2 .

$$\begin{aligned}i(t) &= (-2 \text{ m})e^{-4t} + (2 \text{ m})e^{-1t} \\ &= 2(e^{-1t} - e^{-4t}) \text{ mA}\end{aligned}$$

Therefore, the value of the current $i(t)$ is $\boxed{2(e^{-1t} - e^{-4t}) \text{ mA}}$.